



CALIFORNIA STATE UNIVERSITY
FULLERTONTM

EGEC 180 – Digital Logic and Computer Structures

Spring 2024

Lecture 10: Decoder (2.8.2)

Rakesh Mahto, Ph.D.

Office: E 314, California State University, Fullerton

Office Hour: Monday and Wednesday 2:00 - 3:30 pm

Or by appointment


Office Hour Zoom Meeting ID: 891 2907 5346

Email: ramahto@fullerton.edu

Phone No: 657-278-7274

Decoders

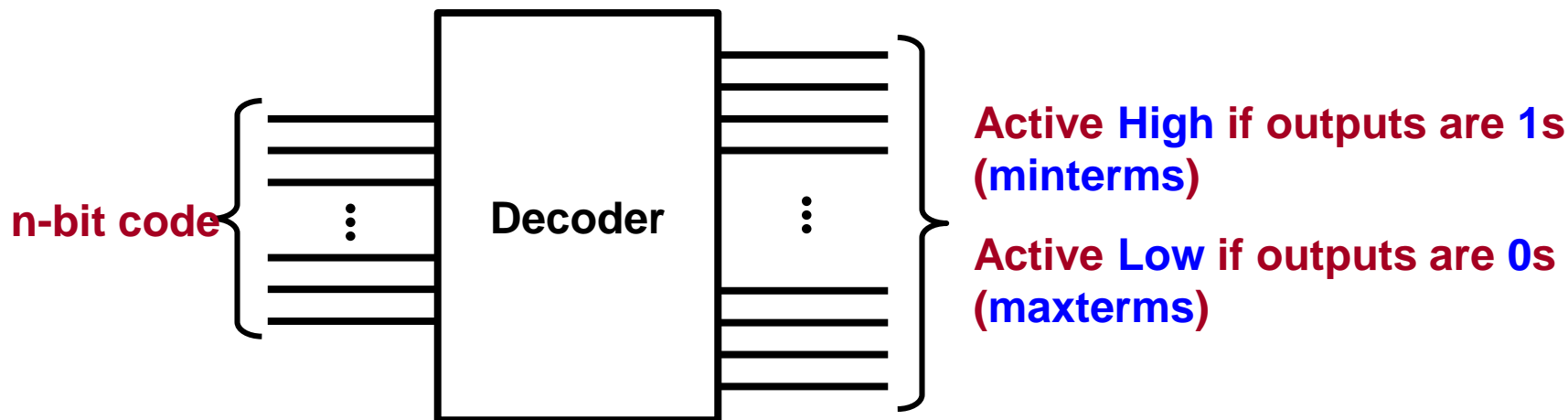Converts n input lines to one of the 2^n different output lines: n -to- 2^n Decoder.



The decoder generates all of the minterms (maxterms) of the n input variables. This means only one of the 2^n output lines will be 1 (or 0) all others will be 0 (or 1) for each combination of the values of the input variables.

If n -bit coded information has “don’t cares”, then the Decoder will output less than 2^n outputs. That is $m \leq 2^n$.

Device Design

We have 4 devices to address, this implies we need only two select lines. This implies we need to design a 2 to 4 decoder

Devices are active LOW

\overline{m}_0 is the CPU

\overline{m}_1 is the Data Memory

\overline{m}_2 is the Video Memory

\overline{m}_3 is the USB Port

E is for the enable line. It is also active Low

Select Lines			Device			
E	A	B	m_0	m_1	m_2	m_3
1	x	x	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

Design Procedure for Decoders

Step 1: Let $k = n$ where we have n inputs and x outputs

Step 2:

if k is even

- Use 2^k AND (NAND) gates driven by two decoders of output size $2^{k/2}$

if k is odd


- Use 2^k AND (NAND) gates driven by two decoders of output size $2^{(k+1)/2}$ and a decoder of output size $2^{(k-1)/2}$

Step 3

Step 3: For each decoder resulting from step 2 repeat step 2 with $k-1$ equal to the values obtained in step 2 until $k = 1$



(Note when $k = 1$ use a 1-to-2 decoder)

A	$m_1 (A')$	$m_2 (A)$
0	1	0
1	0	1

 


2-to-4 Decoder Implementation

  Step 2: k is even ($k=2$) so we will use 2^2 NAND gates.



Transmitting End

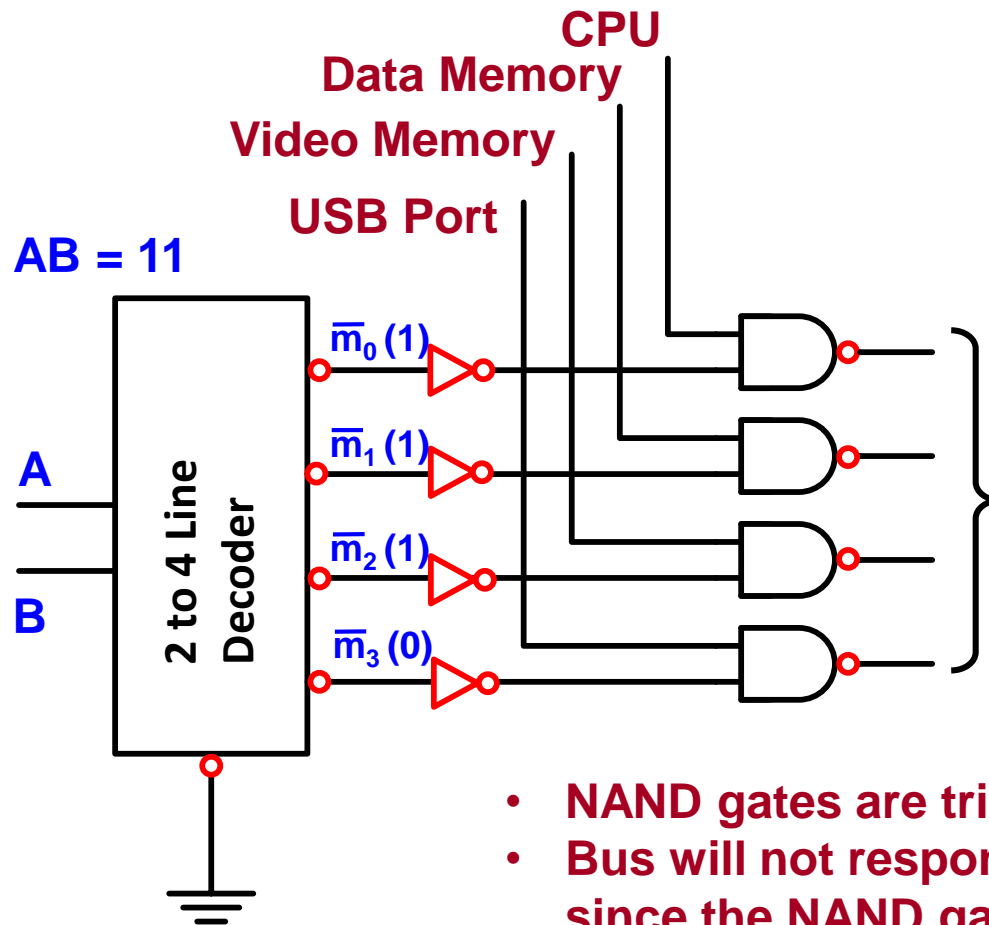

X	Y	NAND Multiplexer
0	0	1
0	1	1
1	0	1
1	1	0

An input of 0 forces the output to be 1 regardless of the other input

this implies Output is always inverted


Inverted Data (1 Bit)

Note: If the USB port writes a 1 the bus gets a 0 and vice versa

- NAND gates are tri-state {0, 1, OPEN}
- Bus will not respond to non-selected devices since the NAND gate has a 0 for one of the inputs

Receiving End

Want the CPU ($AB = 00$) to receive data

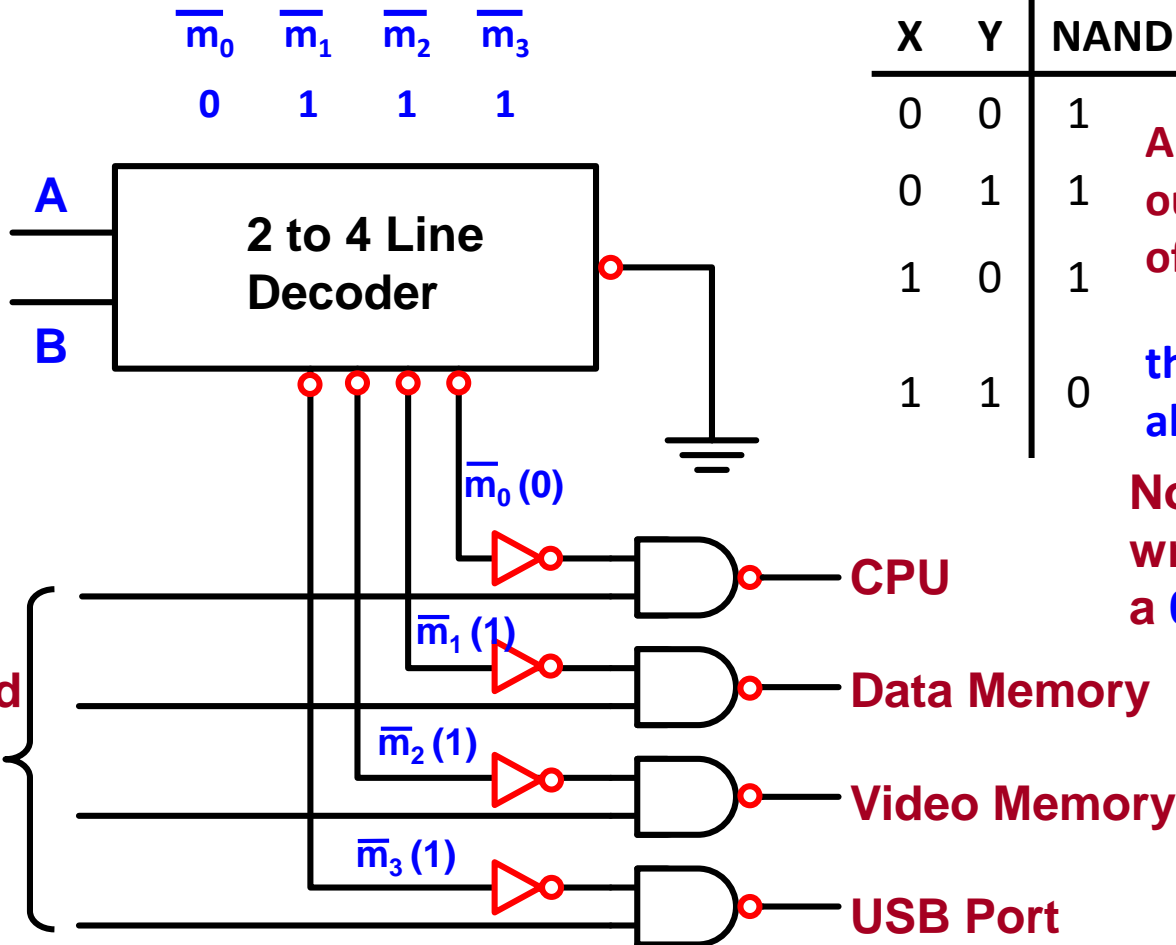

X	Y	NAND Multiplexer
0	0	1
0	1	1
1	0	1
1	1	0

An input of 0 forces the output to be 1 regardless of the other input

this implies Output is always inverted

Note: If the USB port writes a 0 the CPU gets a 0 and vice versa


Circuit Design with Decoders




Example 1 - SOM with Decoder

Given $F_1(A,B,C) = \Sigma m(2,3,5,7)$ – SOM for a) active High outputs, b) active Low outputs (demultiplexer)

A	B	C	F_1	
0	0	0	0	m_0
0	0	1	0	m_1
0	1	0	1	m_2
0	1	1	1	m_3
1	0	0	0	m_4
1	0	1	1	m_5
1	1	0	0	m_6
1	1	1	1	m_7

 


$F_1(A,B,C)$

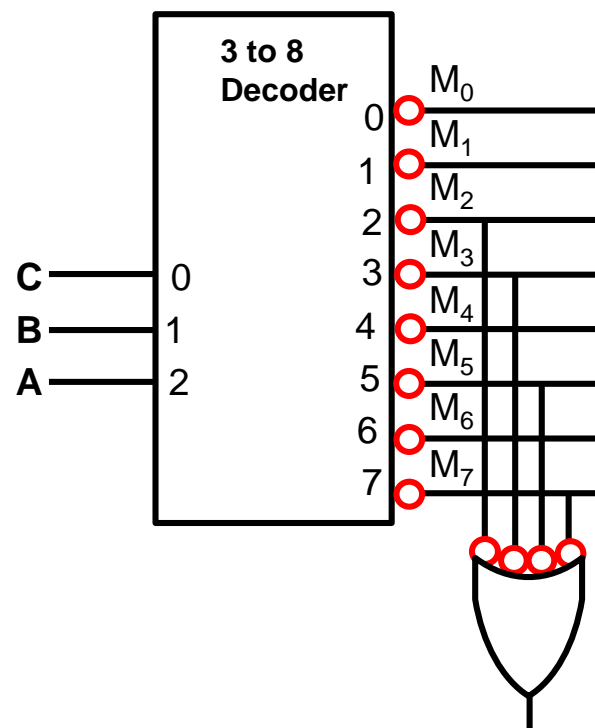

$F_1(A,B,C)$



DeMorgan's Theorem

 

Example 1 - SOM with Decoder


Design of F_1' (A,B,C) = $\Sigma m(0,1,4,6)$ – SOM for a) active High outputs, b) active Low outputs (demultiplexer)

A	B	C	F_1	
0	0	0	0	m_0
0	0	1	0	m_1
0	1	0	1	m_2
0	1	1	1	m_3
1	0	0	0	m_4
1	0	1	1	m_5
1	1	0	0	m_6
1	1	1	1	m_7

  

Using NOR gate since we want the complement F_1

DeMorgan's Theorem

 

Excess-3 to Decimal Decoder



Excess 3 to BCD Decoder Example

Input Excess 3					Output BCD				
A	B	C	D		X	Y	Z	W	
0	0	0	0	m_0	d	d	d	d	
0	0	0	1	m_1	d	d	d	d	
0	0	1	0	m_2	d	d	d	d	
0	0	1	1	m_3	0	0	0	0	0
0	1	0	0	m_4	0	0	0	1	1
0	1	0	1	m_5	0	0	1	0	2
0	1	1	0	m_6	0	0	1	1	3
0	1	1	1	m_7	0	1	0	0	4
1	0	0	0	m_8	0	1	0	1	5
1	0	0	1	m_9	0	1	1	0	6
1	0	1	0	m_{10}	0	1	1	1	7
1	0	1	1	m_{11}	1	0	0	0	8
1	1	0	0	m_{12}	1	0	0	1	9
1	1	0	1	m_{13}	d	d	d	d	
1	1	1	0	m_{14}	d	d	d	d	
1	1	1	1	m_{15}	d	d	d	d	

Note You need 4 decoders one for X, Y, Z, and W

These functions can either implemented using 4 logic circuits or with 4 decoders

Digits

$$X = \sum m(11,12) + \sum d(0,1,2,13,14,15)$$

$$Y = \sum m(7,8,9,10) + \sum d(0,1,2,13,14,15)$$

$$Z = \sum m(5,6,9,10) + \sum d(0,1,2,13,14,15)$$

$$W = \sum m(4,6,8,10,12) + \sum d(0,1,2,13,14,15)$$

Designing the Logic Circuits


$$X = \sum m(11,12) + \sum d(0,1,2,13,14,15)$$

$$Y = \sum m(7,8,9,10) + \sum d(0,1,2,13,14,15)$$

Using maxterms

CD \ AB		CD			
		C'D' 00	C'D 01	CD 11	CD' 10
A'B'	00	X	X	0	X
A'B	01	0	0	0	0
AB	11	1	X	X	X
AB'	10	0	0	1	0


$$X(A,B,C,D) = A(B+C)(B+D)$$

 

Using maxterms

CD \ AB		CD			
		C'D' 00	C'D 01	CD 11	CD' 10
A'B'	00	X	X	0	X
A'B	01	0	0	1	0
AB	11	0	X	X	X
AB'	10	1	1	0	1

$$Y(A,B,C,D) = (A'+C)(B'+D)(B+C'+D')$$

 


Designing the Logic Circuits

$$Z = \sum m(5,6,9,10) + \sum d(0,1,2,13,14,15) \quad \text{Using maxterms}$$

AB \ CD		CD			
		C'D'	C'D	CD	CD'
A'B'	00	X	X	0	X
	01	0	1	0	1
AB	11	0	X	X	X
	10	0	1	0	1

$$X(A,B,C,D) = (C+D)(C'+D')$$

 


Using maxterms

AB \ CD		CD			
		C'D'	C'D	CD	CD'
A'B'	00	X	X	0	X
	01	1	0	0	1
AB	11	1	X	X	X
	10	1	0	0	1



$$W(A,B,C,D) = D'$$

The Finally

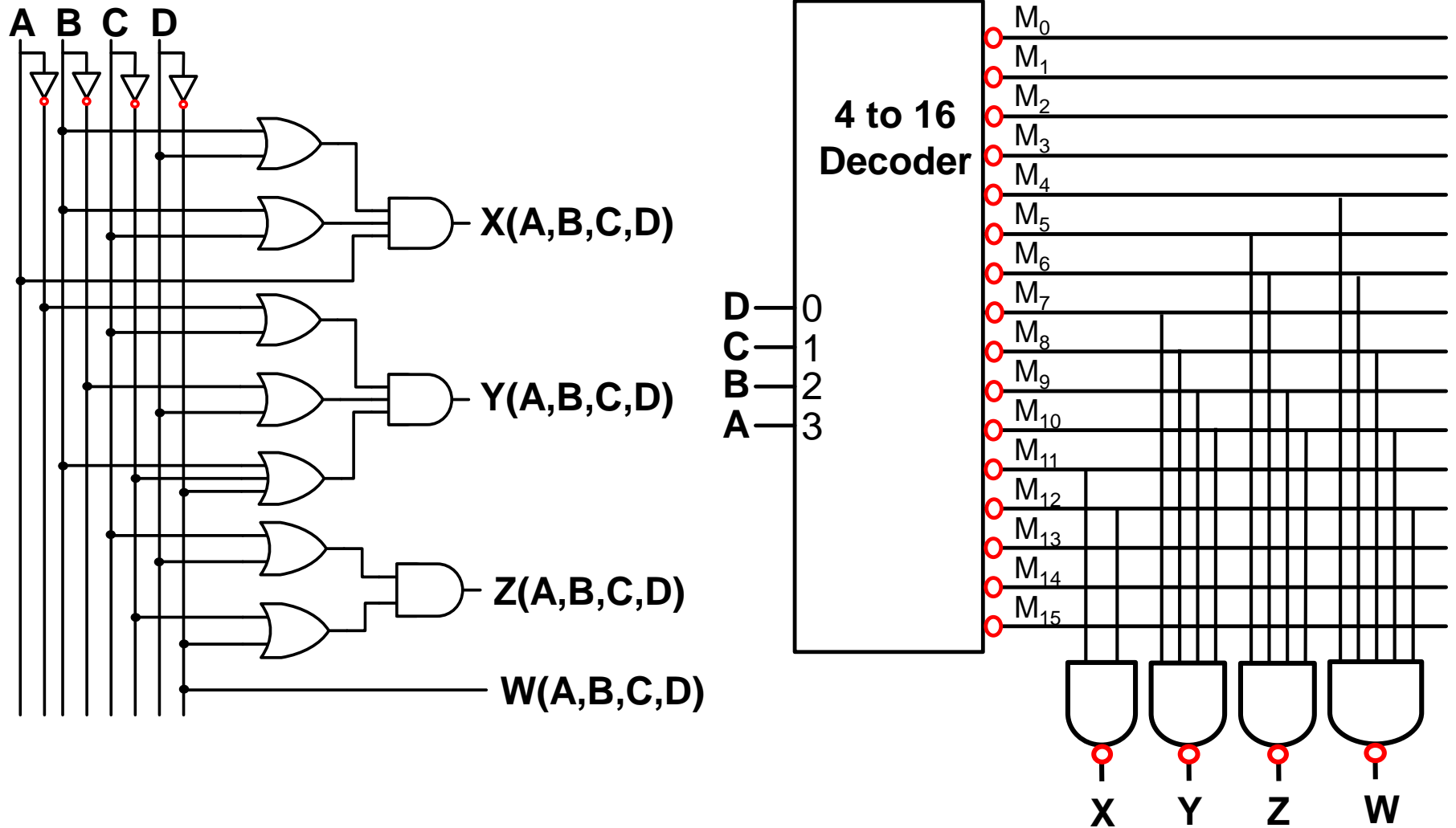

Food For Thought

  Although this may be simpler. It implies a lot of circuitry (a lot of power consumed)



b) Excess-three-to-decimal decoder

Q&A

