

CALIFORNIA STATE UNIVERSITY, FULLERTON
Computer Engineering

EGCP 180 – Digital Logic and Computer Structures
(Fall 2017)

Midterm Exam 2 (Total Points = 45)

(Time allowed: 9:00 — 11:00 AM)

Academic Dishonesty Policy

In line with University policies, the Computer Engineering program supports a strict and well-defined policy against academic dishonesty. Thus, to assure a fair and equitable testing environment for all students, there will be zero tolerance during exam for any of the following:

- Cheating of any type (looking at or copying another student's answers) or helping another student with answers.
- Use of notes, phones, or other aids (other than that allowed by instructor)
- Talking or texting during exams
- Leaving the classroom during the exam (without permission)


Consequences for violating these policies will be a "zero" on the exam at a minimum, with the possibility of an F in the course.

Only one page of handwritten notes (two side), pens/pencils, erasers, and a calculator (shouldn't be necessary) are allowed with the exam.

Normally, full credit is given only if work is shown when appropriate.

 1. (10 Points) Decoder


Design a circuit for the function $F(X, Y, Z) = \prod M(0, 2, 7)$ with a 3-to-8 decoder with active high outputs.



2. (10 Points) Multiplexer


Obtain a MUX design for the $F(A, B, C, D) = \sum m(2, 3, 6, 7, 8, 9, 12, 13)$ such that B, C, and D are connected to the control inputs of Mux. Connect 1's, 0's, A, and \bar{A} to each data input. (Show your steps)

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

 

 3. (10 Points) Extra Credit (Optional)



Repeat question 2 but this time use technique 2 which uses K-map such that B and D are connected to the control inputs of Mux. Connect 1's, 0's, A and C to each data inputs. (Show your steps)





AC\BD	00	01	10	11
00	0	0	0	0
01	1	1	1	1
10	1	1	1	1
11	0	0	0	0

4. (10 Points) Latches and Flip Flop

  - a) Complete the following timing diagram for an NOR based S-R latch. Assume Q begins at 1.




  - b) Complete the following diagrams for the rising-edge-triggered D flip-flop. Assume Q begins at 1.



5. (15 Points) Counter Design

Design a two bit counter shown below

 

a) Fill the state table:


Present State		Next State	
Q1	Q0	Q1 ⁺	Q0 ⁺
0	0	1	0
0	1	0	0
1	0	1	1
1	1	0	1

b) Drive the logic equation of

$$Q1^+ = \overline{Q0}$$

$$Q0^+ = Q1$$

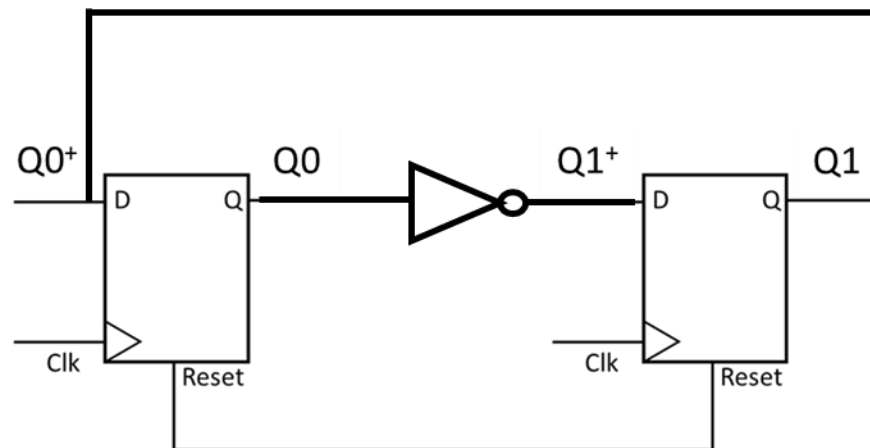c) Complete the logic diagram based on the logic equation



Name: _____

CWID: _____

Date: _____