



EGEC 180 – Digital Logic and Computer Structures

Spring 2024

Lecture 3: Logic Gates (1.5)

Rakesh Mahto, Ph.D.

Office: E 314, California State University, Fullerton

Office Hour: Monday and Wednesday 2:00 - 3:30 pm

Or by appointment

Office Hour Zoom Meeting ID: 891 2907 5346

Email: ramahto@fullerton.edu

Phone No: 657-278-7274

Logical Gates




Basic Operations

- The basic operations of Boolean Algebra are AND, OR, and complement (also known as the Inverse or NOT operations)
- Operator precedence: **Parentheses, NOT, AND, OR**
- **Inverse** or **NOT** or **Negation** or **Complement**
 - So here, we formally state that the complement of “0” is “1”, complement of “1” is “0”.

Example: Ones Complement arithmetic we flipped the 1s and 0s.

- Symbol a tick mark (') is often used to denote complementation.

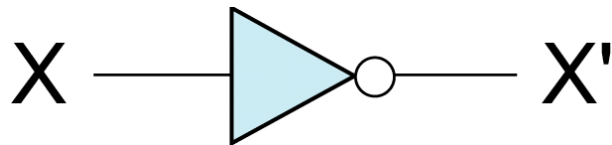Example: if $X = 0$ then $X' = 1$
if $X = 1$ then $X' = 0$




Basic Operations (AND)

- AND operation -> $Z=1$ iff $X=1$ and $Y=1$

if $X=1$ AND $Y=1$ then $Z=1$ else $Z=0$;

When two or more variables are ANDed together, the value of the result will be 1 if and only if (iff) all the variables have the value 1. If any of the variables have the value 0, the result of the AND operation will be 0.

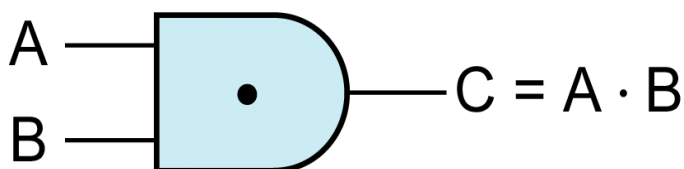- Representation: $XY=Z$, $X \bullet Y=Z$, $X.Y=Z$



Truth Table

A B	C = A · B
0 0	0
0 1	0
1 0	0
1 1	1

Input

Output

Basic Operations (OR)

- OR operation $\rightarrow Z = 0$, iff $X=0$ and $Y=0$
if $X=1$ **OR** $Y=1$ then $Z=1$ else $Z=0$;

When two or more variables are **ORed** together, the value of the result will be **1** if and only if (iff) one or both of the variables have the value **1**. The result of the **OR** operation will be a **0** iff all of the variables have the value **0**.


$$X+Y=Z, \quad X \vee Y=Z$$

Truth Table

A B		C = A + B
0	0	0
0	1	1
1	0	1
1	1	1

Input **Output**

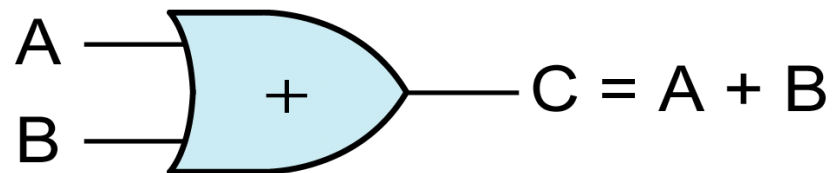NOTE: Binary Logic (Boolean Algebra) \neq Binary Arithmetic



Example Problem #1

- Lets evaluate $XY+Z$

X	Y	Z	XY	XY+Z
0	0	0	$0 \cdot 0 = 0$	$0 + 0 = 0$
0	0	1	$0 \cdot 0 = 0$	$0 + 1 = 1$
0	1	0	$0 \cdot 1 = 0$	$0 + 0 = 0$
0	1	1	$0 \cdot 1 = 0$	$0 + 1 = 1$
1	0	0	$1 \cdot 0 = 0$	$0 + 0 = 0$
1	0	1	$1 \cdot 0 = 0$	$0 + 1 = 1$
1	1	0	$1 \cdot 1 = 1$	$1 + 0 = 1$
1	1	1	$1 \cdot 1 = 1$	$1 + 1 = 1$





Practice Problem #1

- Lets evaluate $X + YZ'$

X	Y	Z	Z'	YZ'	X+YZ'
0	0	0	1	$0 \cdot 1 = 0$	$0 + 0 = 0$
0	0	1	0	$0 \cdot 0 = 0$	$0 + 0 = 0$
0	1	0	1	$1 \cdot 1 = 1$	$0 + 1 = 1$
0	1	1	0	$1 \cdot 0 = 0$	$0 + 0 = 0$
1	0	0	1	$0 \cdot 1 = 0$	$1 + 0 = 1$
1	0	1	0	$0 \cdot 0 = 0$	$1 + 0 = 1$
1	1	0	1	$1 \cdot 1 = 1$	$1 + 1 = 1$
1	1	1	0	$1 \cdot 0 = 0$	$1 + 0 = 1$

Practice Problem #2

- Is $XY+Z = X+YZ'$

$XY+Z$		$X+YZ'$
$0+0 = 0$		$0+0 = 0$
$0+1 = 1$		$0+0 = 0$
$0+0 = 0$		$0+1 = 1$
$0+1 = 1$		$0+0 = 0$
$0+0 = 0$		$1+0 = 1$
$0+1 = 1$		$1+0 = 1$
$1+0 = 1$		$1+1 = 1$
$1+1 = 1$		$1+0 = 1$


So the answer is **NO**

Example Problem #2

- Is $A+B = (A'.B')'$?
- Step 1 Complete the truth table for $A+B$

Step 1	A	B	A'	B'	A'.B'	(A'.B')'
	0	0	1	1	1.1 = 1	0
	0	1	1	0	1.0 = 0	1
	1	0	0	1	0.1 = 0	1
	1	1	0	0	0.0 = 0	1


Step 2	A	B	A+B
	0	0	0
	0	1	1
	1	0	1
	1	1	1

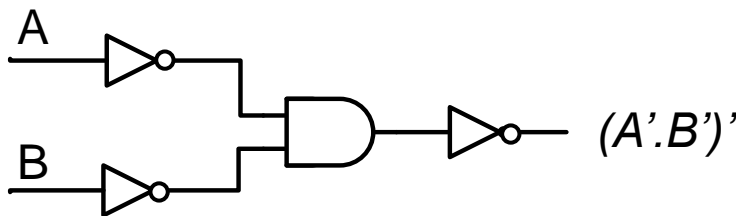


Practice Problem # 3

- Is $AB = (A' + B')'$

A	B	A'	B'	A'+B'	(A'+B')'
0	0	1	1	1+1 = 1	0
0	1	1	0	1+0 = 1	0
1	0	0	1	0+1 = 1	0
1	1	0	0	0+0 = 0	1

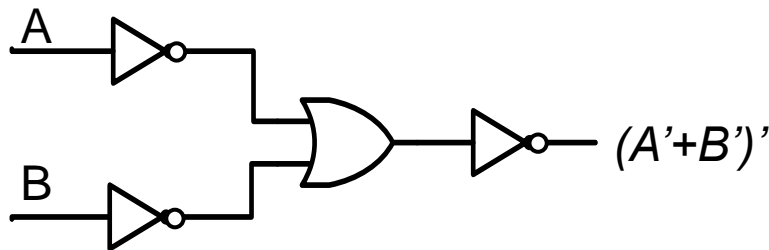


A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

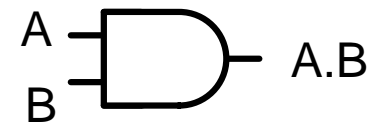

Practice Problem # 4

- What is the output for the function $(X+X').Y$

X	Y	X'	X+X'	$(X+X').Y$
0	0	1	$0+1 = 1$	$1.0=0$
0	1	1	$0+1 = 1$	$1.1=1$
1	0	0	$1+0 = 1$	$1.0=0$
1	1	0	$1+0 = 1$	$1.1=1$



Why implement the circuit It does not change Y?

TABLE 1.1 Major binary operators with variables (or signals) in a Boolean expression

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Boolean expression	Type of operation	VHDL equivalent
\overline{X}	Complement of X	NOT X
$X \cdot Y$	Intersection of X, Y	X AND Y
$X + Y$	Union of X, Y	X OR Y



Operator precedence: parentheses, NOT, AND, OR

Switching Algebra (Switches)

If switch X is open, then we will define the value of X to be 0; if switch X is closed, then we will define the value of X to be 1.

Used with Factory floor automation systems and VHDL Labs.

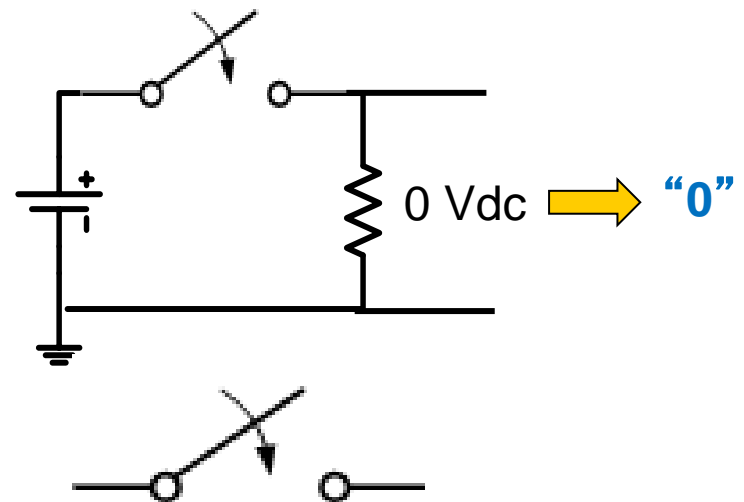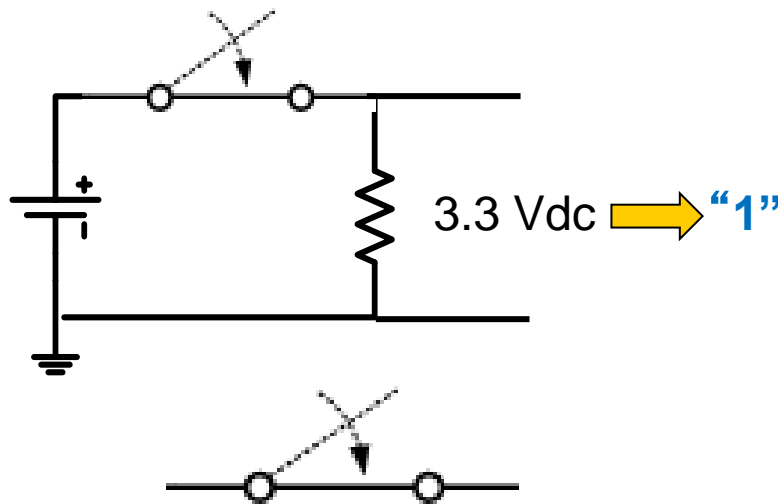Seventh way of playing with Boolean Functions!!!!




Boolean Algebra or Switching Algebra



Switching Algebra (AND)

$$T = AB$$

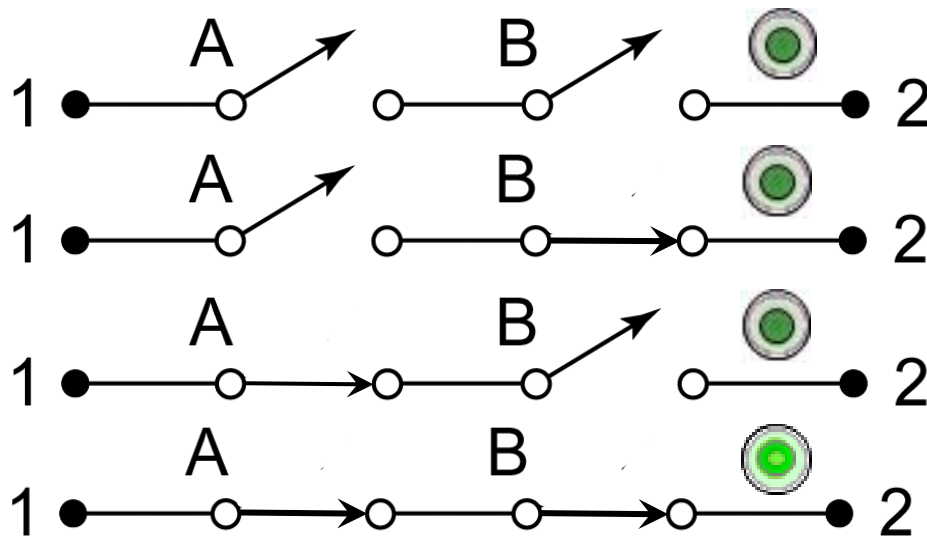


A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

$T = 0$ open circuit between terminals 1 and 2


$T = 1$ closed circuit between terminals 1 and 2

Switching Algebra (OR)


Note: Parallel Structure $T = A+B$

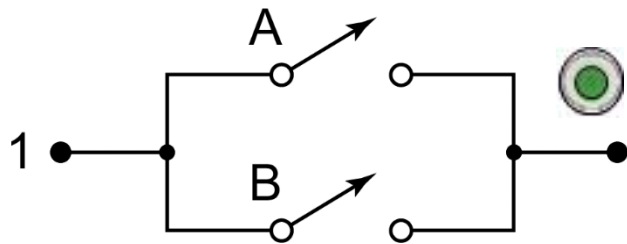


A	B	A+B
0	0	0

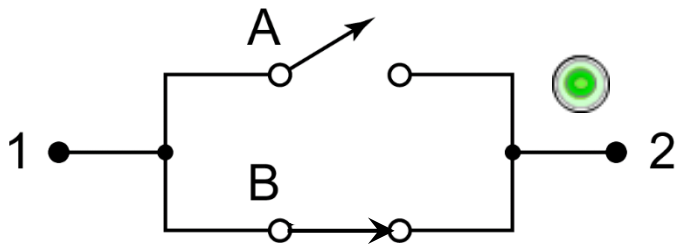

A	B	A+B
0	1	1

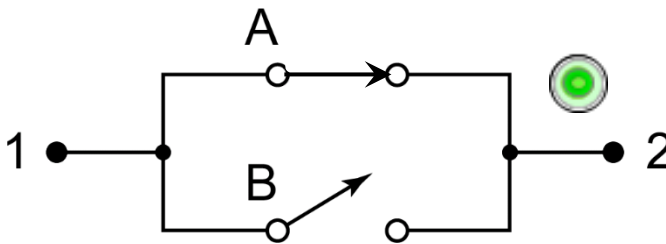

A	B	A+B
1	0	1

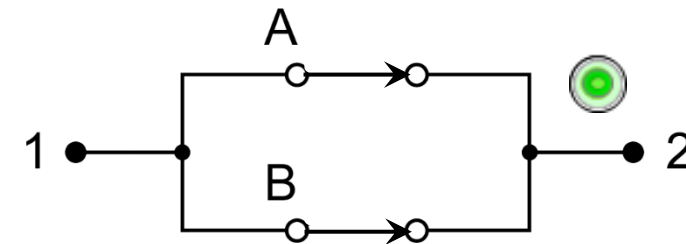


A	B	A+B
1	1	1

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

More on Switching Algebra

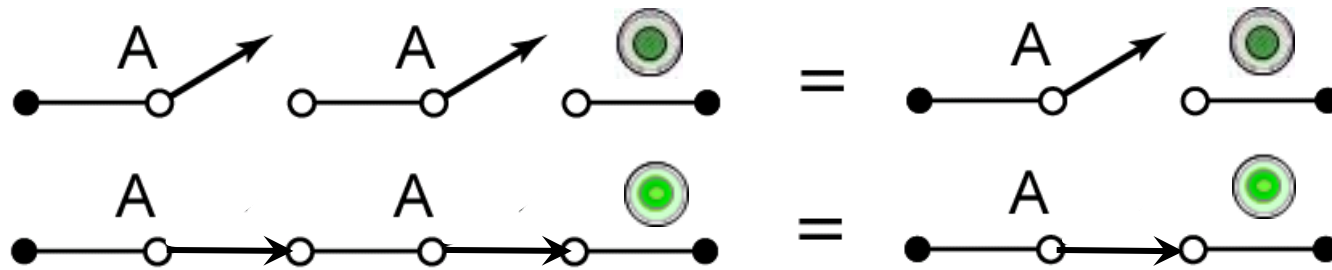
If two switches are both labeled with the variable A , this means that both switches are open when $A = 0$ and both are closed when $A = 1$, thus the following circuits are equivalent:



$$(A \cdot A = A)$$

A	A	$A \cdot A$	} A
0	0	$0 \cdot 0 = 0$	
1	1	$1 \cdot 1 = 1$	

Switching Algebra (OR Idempotent)

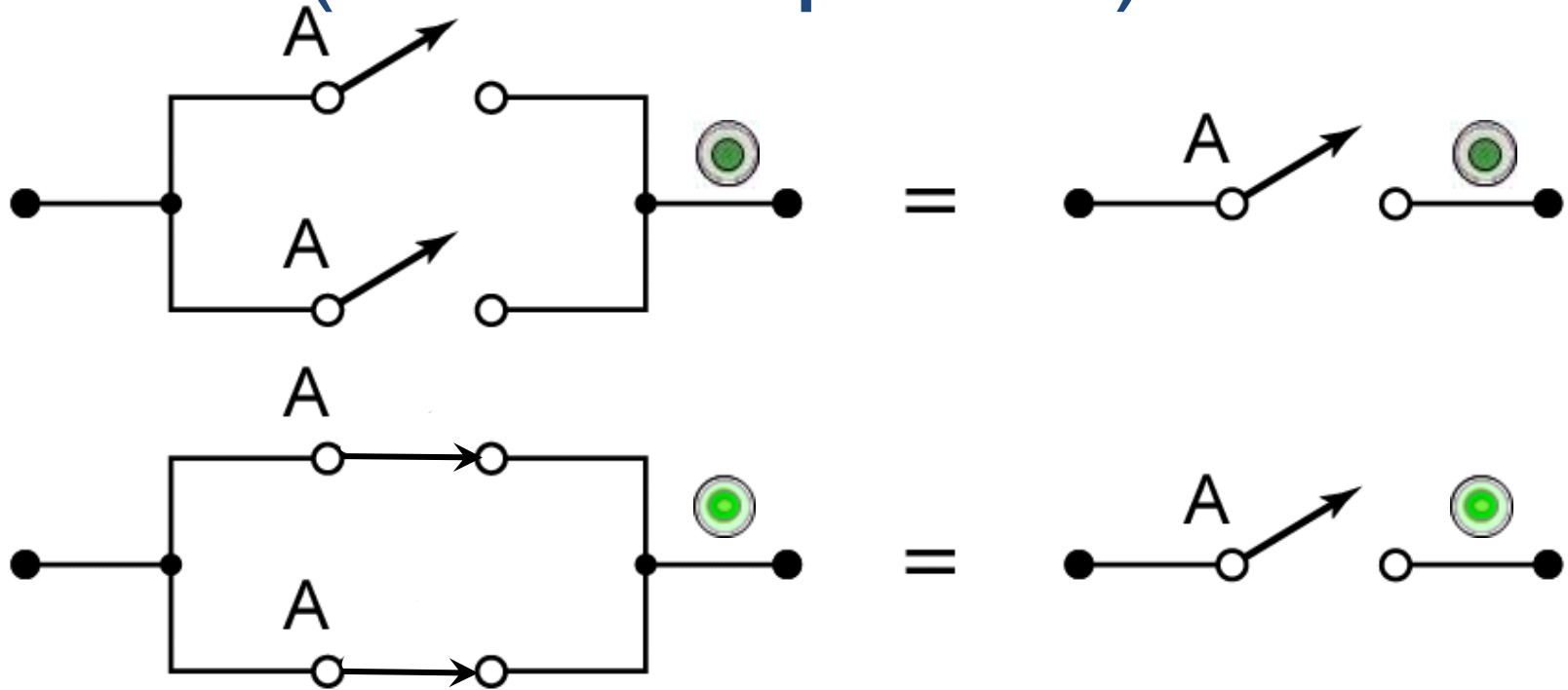


Note: By similar
reasoning
 $A.A = A$

A	A	$A+A$	} A
0	0	$0+0=0$	
1	1	$1+1=1$	

Switching Algebra (Identities)


$$(A + 0 = A)$$

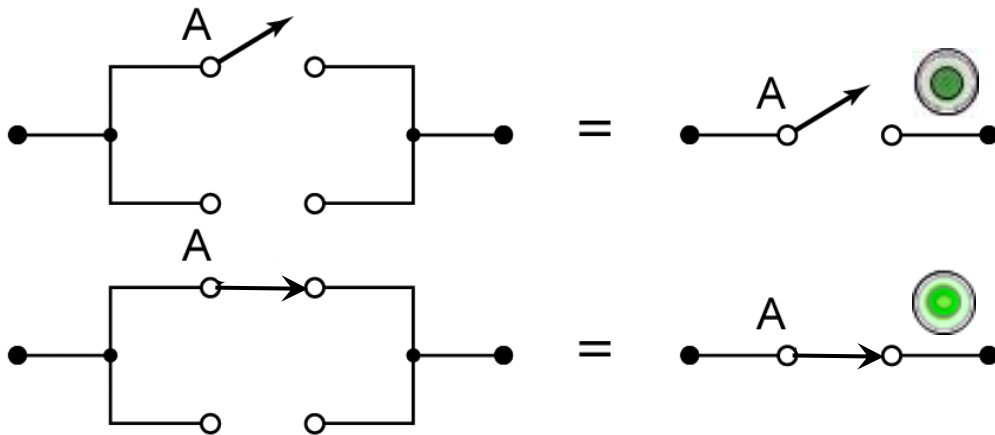

A	0	A+0
0	0	0+0 = 0
1	0	1+0 = 1

} **A**

$$(A + 1 = 1)$$

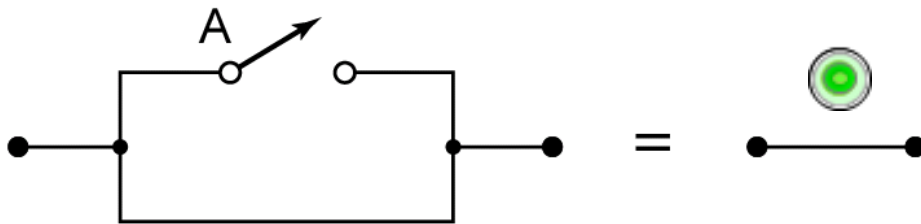


A	1	A+1
0	1	0+1 = 1
1	1	1+1 = 1

} **A**

Switching Algebra (Tautology)

A in parallel with A' can be replaced with a closed circuit because one or the other of the two switches is always closed.

$$(A + A' = 1)$$

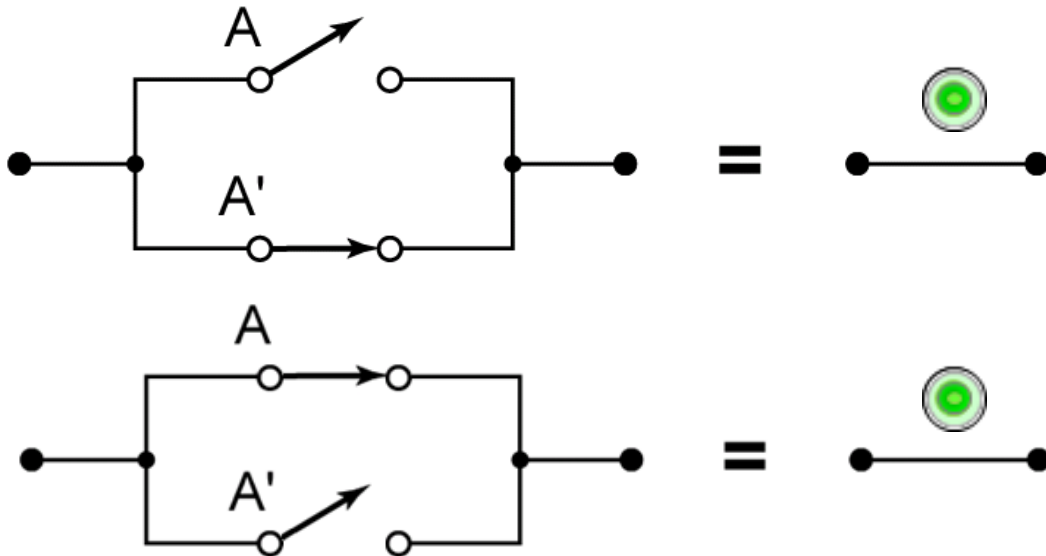


A	A'	$A+A'$
0	1	$0+1=1$
1	0	$1+0=1$

} 1

Switching Algebra (Fallacy)

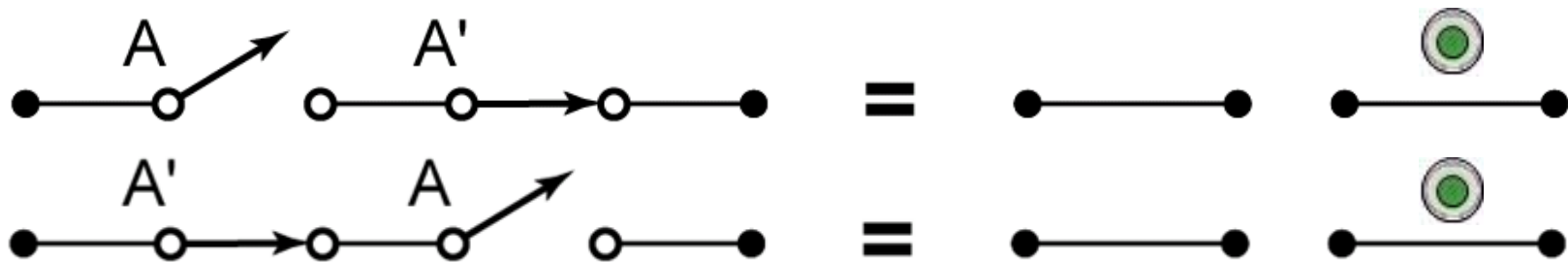Similarly, switch A in series with A' can be replaced with an open circuit because one or the other of the two switches is always open.



$$(A \cdot A' = 0)$$

A	A'	A.A'
0	1	0.1=0
1	0	1.0=0

0

Boolean Algebra Theorems


Absorption Theorem	T1a: $X \cdot (X + Y) = X$ T1b: $X + X \cdot Y = X$	Double Complementation or Double Negation Theorem	T7: $\overline{\overline{X}} = X$
Adjacency Theorem	T2a: $X \cdot Y + X \cdot \overline{Y} = X$ T2b: $(X + Y) \cdot (X + \overline{Y}) = X$	Idempotency Theorem	T8a: $X \cdot X = X$ T8b: $X + X = X$
Associative Theorem	T3a: $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$ T3b: $X + (Y + Z) = (X + Y) + Z$	Identity Element Theorem	T9a: $X \cdot 0 = 0$ T9b: $X + 1 = 1$
Consensus Theorem	T4a: $X \cdot Y + \overline{X} \cdot Z + Y \cdot Z = X \cdot Y + \overline{X} \cdot Z$ T4b: $(X + Y) \cdot (\overline{X} + Z) \cdot (Y + Z) = (X + Y) \cdot (\overline{X} + Z)$	Simplification Theorem	T10a: $X \cdot (\overline{X} + Y) = X \cdot Y$ T10b: $X + \overline{X} \cdot Y = X + Y$

DeMorgan's Theorem (with two variables)	T5a: $\overline{X \cdot Y} = \overline{X} + \overline{Y}$ T5b: $\overline{X + Y} = \overline{X} \cdot \overline{Y}$
DeMorgan's Theorem (with multiple variables)	T6a: $\overline{X \cdot Y \cdot Z \dots} = \overline{X} + \overline{Y} + \overline{Z} + \dots$ T6b: $\overline{X + Y + Z + \dots} = \overline{X} \cdot \overline{Y} \cdot \overline{Z} \cdot \dots$

Comparing circuit complexity for the Boolean functions F1 and F2

In general, it is better to use fewer logic gates to minimize complexity, cost, and power requirements.

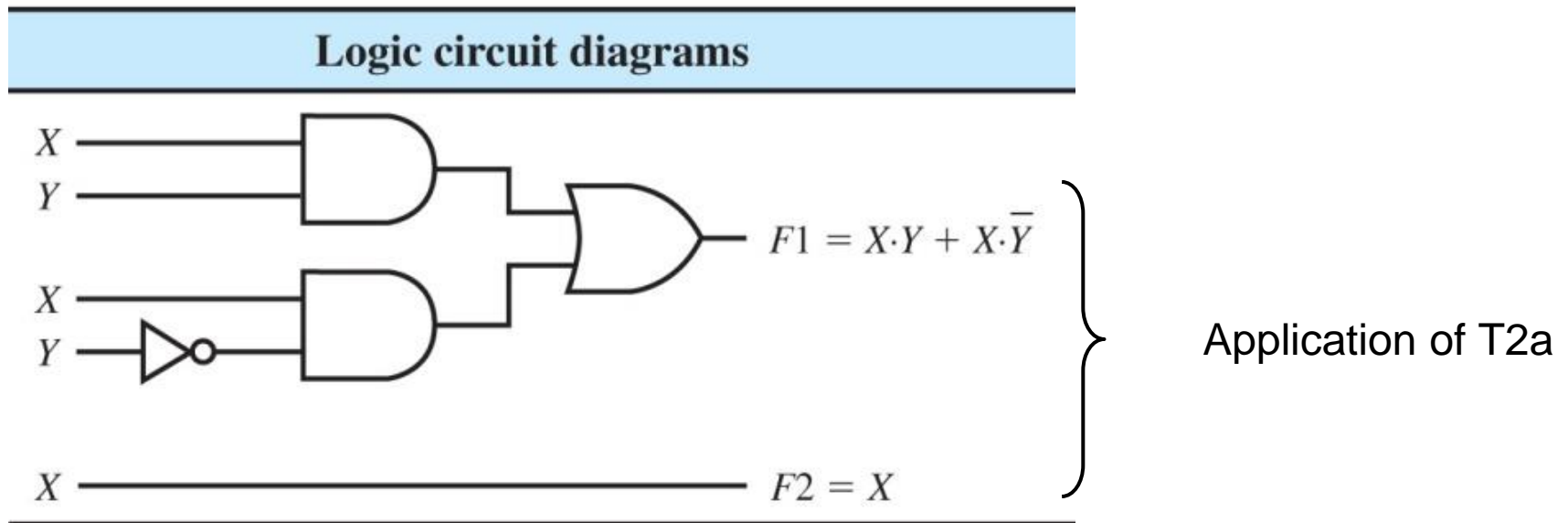Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Adjacency Theorem T2a: $X \cdot Y + X \cdot \bar{Y} = X$

Theorem T2b: $(X + Y) \cdot (X + \bar{Y}) = X$

Proving Boolean Algebra Theorems

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Simplification Theorem T10b: $X + \bar{X} \cdot Y = X + Y$

Proof by perfect induction method

Step 1: Make the truth table

X	Y	\bar{X}	$\bar{X} \cdot Y$	$X + \bar{X} \cdot Y$	$X + Y$
0	0	1	0	0	0
0	1	1	1	1	1
1	0	0	0	1	1
1	1	0	0	1	1

Step 2: Fill in each column in the table using the operator definitions

X	Y	\bar{X}	$\bar{X} \cdot Y$	$X + \bar{X} \cdot Y$	$X + Y$
0	0	1	0	0	0
0	1	1	1	1	1
1	0	0	0	1	1
1	1	0	0	1	1

EOL = EOR

Step 3: Verify that EOL = EOR

Proof by mathematical manipulation method (proving that EOR = EOL)

Substitute postulates and/or theorems to show that EOR = EOL, which can be tricky because it involves trial and error

$$X + Y$$

$$X + Y \cdot 1$$

$$X + Y \cdot (X + \bar{X})$$

$$X + Y \cdot X + Y \cdot \bar{X}$$

$$X \cdot 1 + Y \cdot X + Y \cdot \bar{X}$$

$$X \cdot 1 + X \cdot Y + \bar{X} \cdot Y$$

$$X \cdot (1 + Y) + \bar{X} \cdot Y$$

$$X \cdot 1 + \bar{X} \cdot Y$$

$$X + \bar{X} \cdot Y$$

Note that EOR = EOL

Using the following postulates and/or theorems:

Variable dominate rule

$$P1a: X \cdot 1 = X$$

Complement rule

$$P4b: X + \bar{X} = 1$$

Distributive rule

$$P3a: X \cdot (Y + Z) = X \cdot Y + X \cdot Z$$

Variable dominate rule

$$P1a: X \cdot 1 = X$$

Commutative rule

$$P2a: X \cdot Y = Y \cdot X$$

Distributive rule

$$P3a: X \cdot (Y + Z) = X \cdot Y + X \cdot Z$$

Identity element theorem

$$T9b: X + 1 = 1$$

Variable dominate rule

$$P1a: X \cdot 1 = X$$

Proof of Adjacency Theorem

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Adjacency Theorem T2a: $X \cdot Y + X \cdot \bar{Y} = X$

Proof by perfect induction method

X	Y	\bar{Y}	$X \cdot Y$	$X \cdot \bar{Y}$	$X \cdot Y + X \cdot \bar{Y}$
0	0	1	0	0	0
0	1	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
EOR			=		EOL

Proof by mathematical manipulation method (proving that EOL = EOR)

$$X \cdot Y + X \cdot \bar{Y}$$

$$X \cdot (Y + \bar{Y})$$

$$X \cdot 1$$

$$X$$

$$\text{Note that EOL} = \text{EOR}$$

Using the following postulates and/or theorems:

Distributive rule

Complement rule

Variable dominate rule

$$\text{P3a: } X \cdot (Y + Z) = X \cdot Y + X \cdot Z$$

$$\text{P4b: } X + \bar{X} = 1$$

$$\text{P1a: } X \cdot 1 = X$$

Boolean Functions and Truth Tables



Truth Table

We can use a Truth Table to specify the output values of a circuit of logic gates in terms of the values of the input variables.

If an expression has n variables and each variable can have the value 0 or 1, the number of different combinations of values of the variables is 2^n .

Thus, a Truth Table for an n -variable expression will have n columns and 2^n rows.

Two expressions are equal if they have the same value for every possible combination of the variables.

Truth Table for 3 variables

Since the expression $(A + C)(B' + C)$ has the same value as $AB' + C$ for all eight combinations of values of the variables A, B, and C, we conclude that:

$$AB' + C = (A + C)(B' + C)$$

A B C	B'	AB'	AB'+C		A+C	B'+C	(A+C)(B'+C)
0 0 0	1	0.1=0	0+0=0		0+0=0	1+0=1	0.1=0
0 0 1	1	0.1=0	0+1=1		0+1=1	1+1=1	1.1=1
0 1 0	0	0.0=0	0+0=0		0+0=0	0+0=0	0.0=0
0 1 1	0	0.0=0	0+1=1		0+1=1	0+1=1	1.1=1
1 0 0	1	1.1=1	0+1=1		1+0=1	0+1=1	1.1=1
1 0 1	1	1.1=1	1+1=1		1+1=1	1+1=1	1.1=1
1 1 0	0	1.0=0	0+0=0		1+0=1	0+0=0	1.0=0
1 1 1	0	1.0=0	1+0=1		1+1=1	0+1=1	1.1=1


Other Operations (exclusive OR)

- Exclusive OR (XOR) operation $\rightarrow Z = 1$, iff $X \neq Y$

if $X \neq Y$ then $Z=1$ else $Z=0$;

When two or more variables are **XORed** together, the value of the result will be **1** if and only if (iff) they are not the same of the. The result of the **XOR** operation will be a **0** iff both have the same value.
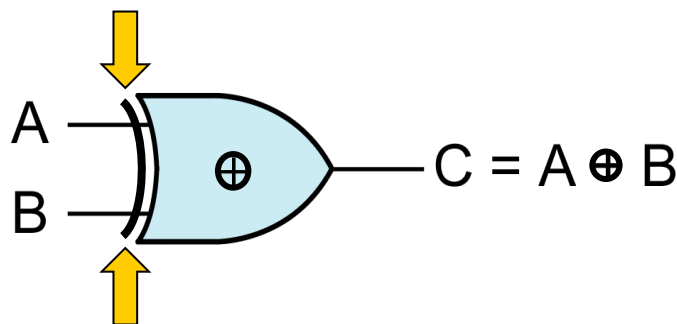
$$X \text{ xor } Y = Z, \quad X \oplus Y = Z, \quad XY' + X'Y = Z, \quad X\bar{Y} + \bar{X}Y = Z$$



Note: the Extra line

Truth Table

Boolean	X Y		$X \oplus Y$
	$X'Y'$	0 0	0
	$X'Y$	0 1	1
	XY'	1 0	1
	XY	1 1	0

Truth
Function
 $Z = X.Y' + X'.Y$

Input


Output

Basic Operations (Not AND)

- Not AND (NAND) operation -> $Z=0$ iff $X=1$ and $Y=1$
if $X=0$ AND $Y=0$ then $Z=1$ else $Z=0$;

When two or more variables are Nanded together, the value of the result will be 1 if and only if (iff) all the variables have the value 0. If any of the variables have the value 1, the result of the NAND operation will be 0.

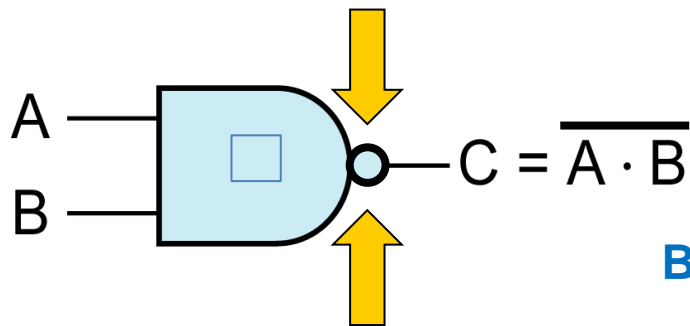- Representation: $\underline{XY}=Z$, $\underline{X \bullet Y}=Z$, $\underline{(X.Y)'}=Z$



Note: the Negation or Inversion Bubble

Truth Table

	X	Y	\overline{XY}
$X' Y'$	0	0	1
$X' Y$	0	1	1
$X Y'$	1	0	1
$X Y$	1	1	0

Boolean

Truth
Function

$$Z = X' Y' + X' Y + X Y'$$


Input

Output

Basic Operations (Not OR)

- Not OR or NOR operation $\rightarrow Z = 1$, iff $X=0$ and $Y=0$
if $X=1$ **OR** $Y=1$ then $Z=0$ else $Z=1$;

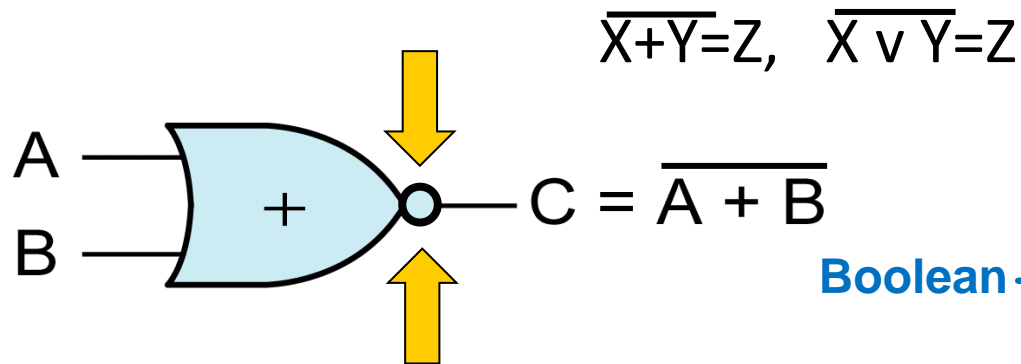When two or more variables are **NORed** together, the value of the result will be **1** if and only if (iff) both of the variables have the value 0. The result of the **NOR** operation will be a **1** iff any of the variables have the value **1**.



Note: the Negation or Inversion Bubble

Truth Table

		X	Y	$\overline{X+Y}$	Truth Function
Boolean		$X'Y'$	0 0	1	
		$X'Y$	0 1	0	$\rightarrow Z=X'Y'$
		XY'	1 0	0	
		XY	1 1	0	

Input

Output

Q&A

