



# EGEC 180 – Digital Logic and Computer Structures

Spring 2024

Lecture 7: Extra Example

*Rakesh Mahto, Ph.D.*

**Office:** E 314, California State University, Fullerton

**Office Hour:** Monday and Wednesday 2:00 - 3:30 pm

*Or by appointment*

**Office Hour Zoom Meeting ID:** 891 2907 5346

**Email:** [ramahto@fullerton.edu](mailto:ramahto@fullerton.edu)

**Phone No:** 657-278-7274

# Example Problem #1

- Lets evaluate  $XY+Z$

X	Y	Z	XY	XY+Z
0	0	0	$0 \cdot 0 = 0$	$0 + 0 = 0$
0	0	1	$0 \cdot 0 = 0$	$0 + 1 = 1$
0	1	0	$0 \cdot 1 = 0$	$0 + 0 = 0$
0	1	1	$0 \cdot 1 = 0$	$0 + 1 = 1$
1	0	0	$1 \cdot 0 = 0$	$0 + 0 = 0$
1	0	1	$1 \cdot 0 = 0$	$0 + 1 = 1$
1	1	0	$1 \cdot 1 = 1$	$1 + 0 = 1$
1	1	1	$1 \cdot 1 = 1$	$1 + 1 = 1$





# Practice Problem #1

- Lets evaluate  $X + YZ'$

X	Y	Z	Z'	YZ'	X+YZ'
0	0	0	1	$0 \cdot 1 = 0$	$0 + 0 = 0$
0	0	1	0	$0 \cdot 0 = 0$	$0 + 0 = 0$
0	1	0	1	$1 \cdot 1 = 1$	$0 + 1 = 1$
0	1	1	0	$1 \cdot 0 = 0$	$0 + 0 = 0$
1	0	0	1	$0 \cdot 1 = 0$	$1 + 0 = 1$
1	0	1	0	$0 \cdot 0 = 0$	$1 + 0 = 1$
1	1	0	1	$1 \cdot 1 = 1$	$1 + 1 = 1$
1	1	1	0	$1 \cdot 0 = 0$	$1 + 0 = 1$

# Practice Problem #2

- Is  $XY+Z = X+YZ'$

$XY+Z$		$X+YZ'$
$0+0 = 0$		$0+0 = 0$
$0+1 = 1$		$0+0 = 0$
$0+0 = 0$		$0+1 = 1$
$0+1 = 1$		$0+0 = 0$
$0+0 = 0$		$1+0 = 1$
$0+1 = 1$		$1+0 = 1$
$1+0 = 1$		$1+1 = 1$
$1+1 = 1$		$1+0 = 1$



So the answer is **NO**

# Example Problem #2

- Is  $A+B = (A'.B')'$ ?
- Step 1 Complete the truth table for  $A+B$
- Step 2 Evaluate the Truth Table for  $(A'.B')'$

A	B	A'	B'	A'.B'	(A'.B')'
0	0	1	1	1.1 = 1	0
0	1	1	0	1.0 = 0	1
1	0	0	1	0.1 = 0	1
1	1	0	0	0.0 = 0	1


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

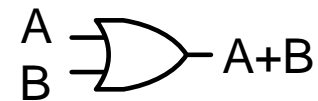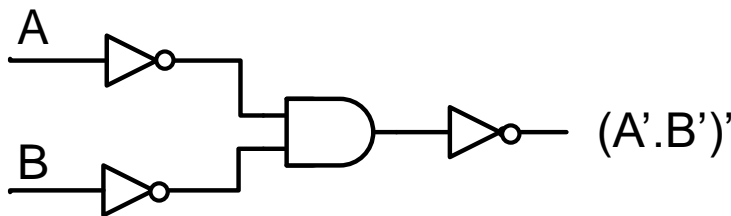


# Practice Problem # 3

- Is  $AB = (A' + B')'$

A	B	A'	B'	A'+B'	(A'+B')'
0	0	1	1	1+1 = 1	0
0	1	1	0	1+0 = 1	0
1	0	0	1	0+1 = 1	0
1	1	0	0	0+0 = 0	1

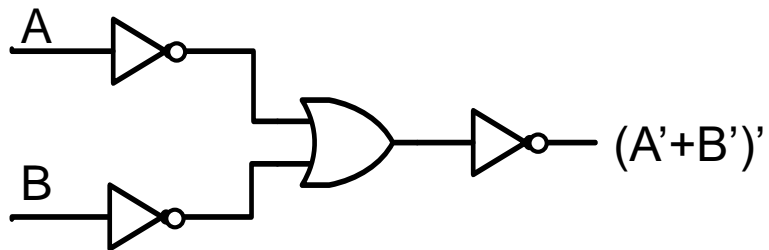


A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

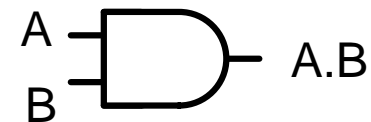

# Practice Problem # 4

- What is the output for the function  $(X+X').Y$

X	Y	X'	$X+X'$	$(X+X').Y$
0	0	1	$0+1 = 1$	$1.0=0$
0	1	1	$0+1 = 1$	$1.1=1$
1	0	0	$1+0 = 1$	$1.0=0$
1	1	0	$1+0 = 1$	$1.1=1$




**Why implement the circuit It does not change Y?**

# Practice Problem #1

Given the following truth table write the truth function for F1?

A	B	C	F1
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

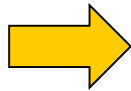

	A	B	C	F1
$A'B'C'$	0	0	0	0
$A'B'C$	0	0	1	0
$A'BC'$	0	1	0	0
$A'BC$	0	1	1	0
$AB'C'$	1	0	0	1
$AB'C$	1	0	1	1
$ABC'$	1	1	0	1
$ABC$	1	1	1	0

Truth  
Function


$$F1 = AB'C' + AB'C + ABC'$$



# Practice Problem #2

Given the following truth table write the truth function for F2?

A	B	C	F2
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

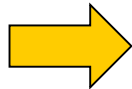

	A	B	C	F2
$A'B'C'$	0	0	0	1
$A'B'C$	0	0	1	1
$A'BC'$	0	1	0	1
$A'BC$	0	1	1	1
$AB'C'$	1	0	0	0
$AB'C$	1	0	1	0
$ABC'$	1	1	0	1
$ABC$	1	1	1	0


Truth  
Function

$$F2 = A'B'C' + A'B'C + A'BC' + A'BC + ABC'$$

# Practice Problem #3

Given the following truth table write the truth function for F1?

A	B	C	D	F3
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

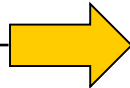

	A	B	C	D	F3
A'B'C'D'	0	0	0	0	1
A'B'C'D	0	0	0	1	1
A'B'CD'	0	0	1	0	1
A'B'CD	0	0	1	1	1
A'BC'D'	0	1	0	0	0
A'BC'D	0	1	0	1	0
A'BCD'	0	1	1	0	1
A'BCD	0	1	1	1	0
AB'C'D'	1	0	0	0	1
AB'C'D	1	0	0	1	1
AB'CD'	1	0	1	0	1
AB'CD	1	0	1	1	1
ABC'D'	1	1	0	0	0
ABC'D	1	1	0	1	0
ABCD'	1	1	1	0	1
ABCD	1	1	1	1	0


Truth  
Function

$$F3 = A'B'C'D' + A'B'C'D + A'B'CD' + A'B'CD + A'BCD' + AB'C'D + AB'CD' + ABCD'$$

# Expressions/Boolean Functions

- A literal means we need to provide a wire to move the signal to the gate.
  - Each appearance of a variable or its complement in an expression will be referred to as a **literal**.
  - Thus, each literal in an expression corresponds to a gated input.



Gates are the Boolean operations

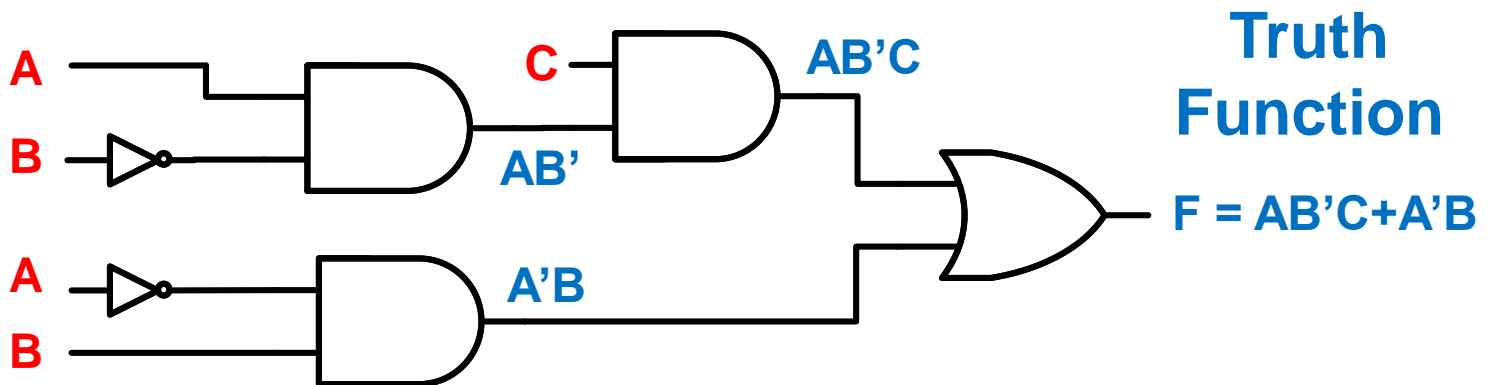

$AB'C + A'B$ : 3 variables, 5 literals, 6 Gates
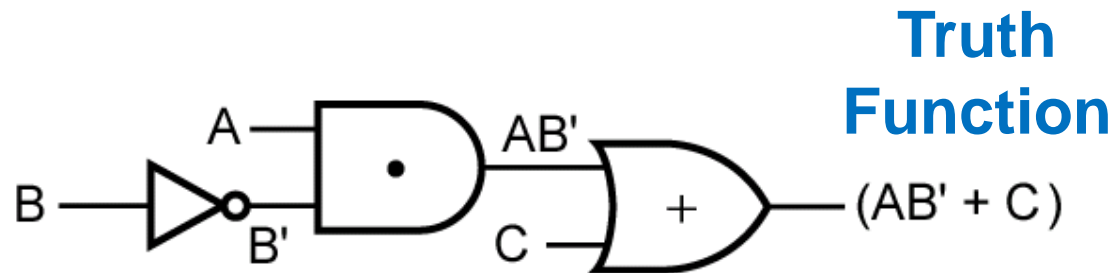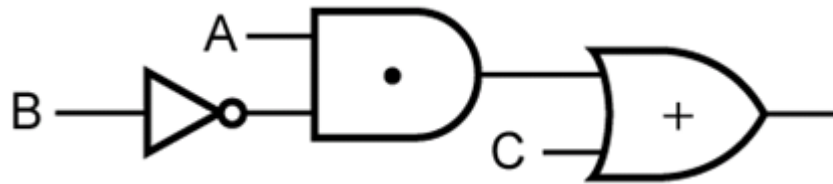
# Practice Problem #4


What is this systems SOM Function and What is the number of variable, literals, and gates?



$AB' + C$ : 3 variables, 3 literals, 3 Gates
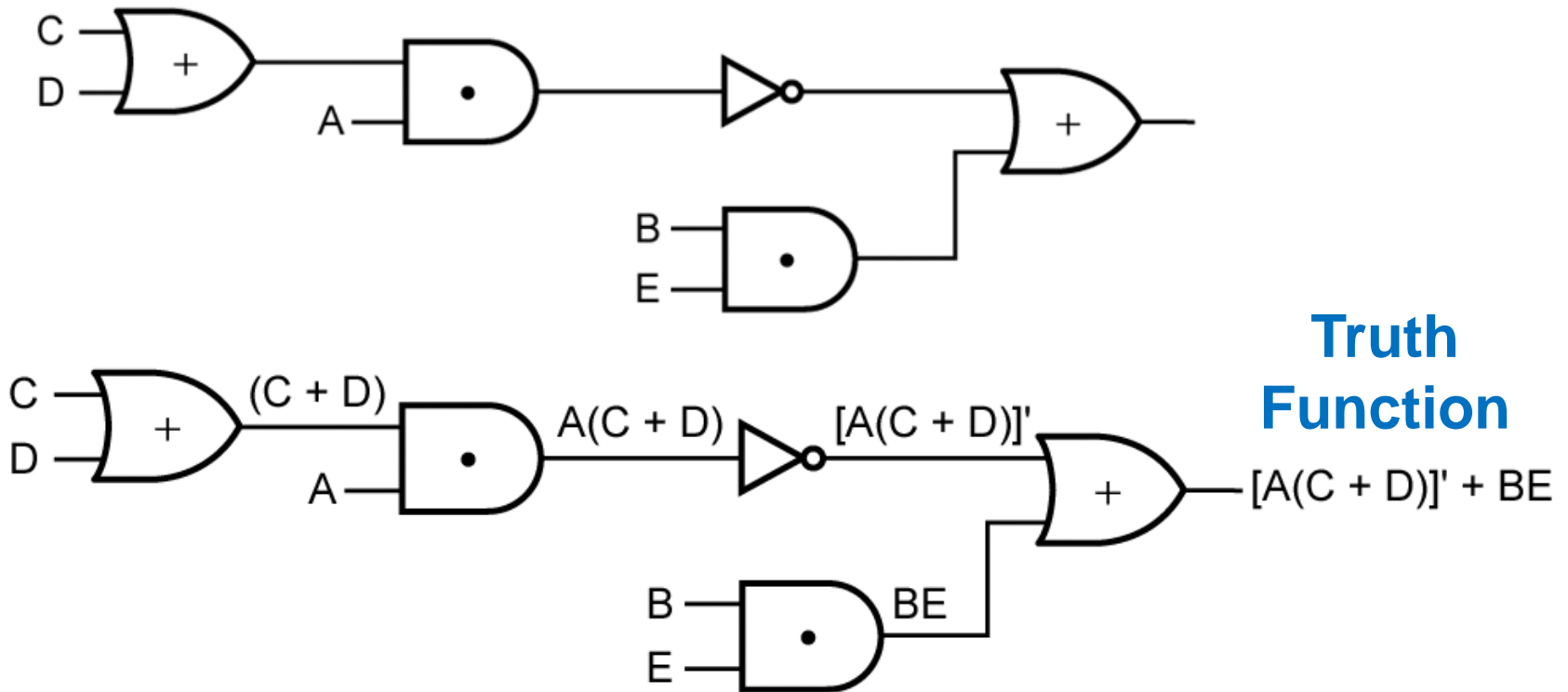
# Practice Problem #5

What is this systems SOM Function and What is the number of variable, literals, and gates?




$(A(C + D))' + BE$ : 5 variables, 5 literals, 5 Gates

# Practice Problem #6

Given the following truth table Draw the Gate Logic?

A	B	C	F1
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

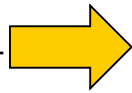


	A	B	C	F1
$A'B'C'$	0	0	0	0
$A'B'C$	0	0	1	0
$A'BC'$	0	1	0	0
$A'BC$	0	1	1	0
$AB'C'$	1	0	0	1
$AB'C$	1	0	1	1
$ABC'$	1	1	0	1
$ABC$	1	1	1	0

Truth  
Function

$$F1 = AB'C' + AB'C + ABC'$$

Truth  
Function


$$F1 = AB'C' + AB'C + ABC'$$

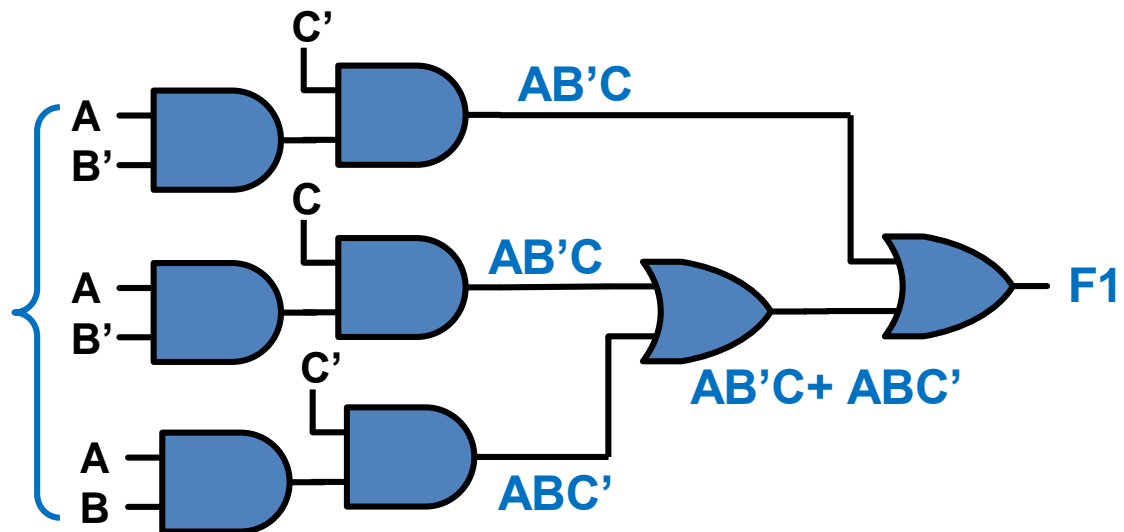

# Practice Problem #7

Given the following truth table write the truth function for F2?

A	B	C	F2
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

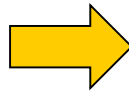


	A	B	C	F2
$A'B'C'$	0	0	0	1
$A'B'C$	0	0	1	1
$A'BC'$	0	1	0	1
$A'BC$	0	1	1	1
$AB'C'$	1	0	0	0
$AB'C$	1	0	1	0
$ABC'$	1	1	0	1
$ABC$	1	1	1	0

Truth  
Function

$$F2 = A'B'C' + A'B'C + A'BC' + A'BC + ABC'$$

Truth  
Function
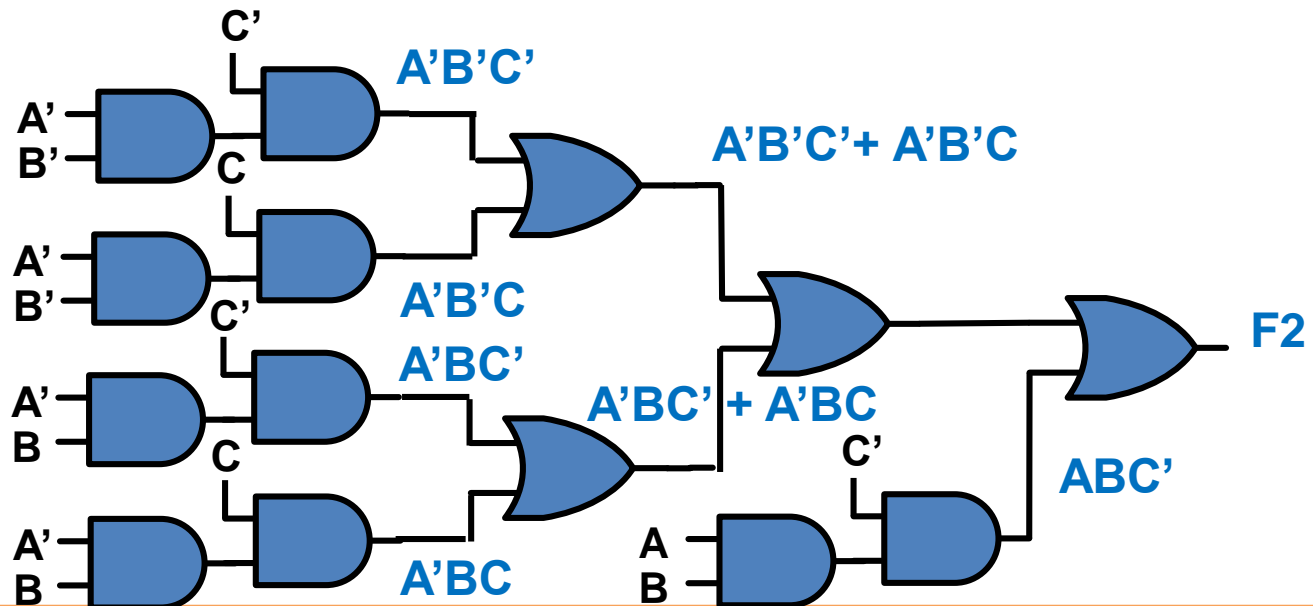
$$F2 = A'B'C' + A'B'C + A'BC' + A'BC + ABC'$$



# Q&A

