



CALIFORNIA STATE UNIVERSITY
FULLERTON[™]

EGEC 180: – Digital Logic and Computer Structures

Spring 2024

Lecture 14: Midterm Exam No 2 Review

Rakesh Mahto, Ph.D.

Office: E 314, California State University, Fullerton

Office Hour: Monday and Wednesday 2:00 - 3:30 pm

Or by appointment

Office Hour Zoom Meeting ID: 891 2907 5346

Email: ramahto@fullerton.edu

Phone No: 657-278-7274

Mid-Term Exam No 2

- Day: 1 May 2014
- Time: 11:30 8:00 AM
- Lecture Slides from 8 to 13
- Bring a cheat-sheet of one page (A4 Size), pen, pencil and calculator.

OR/AND to NOR/NOR

(Practice Problem #3)


Given $F_2(X,Y,Z) = X'Z' + XZ + Y$

1. Find a minimum *product-of-sum* expression for F using a Karnaugh Map

		YZ			
		Y'Z'	Y'Z	YZ	YZ'
X	X'	00	01	11	10
	0	1	0	1	1
X	1	0	1	1	1

$$F_2(X,Y,Z) = (X+Y+Z')(X'+Y+Z)$$

 
2. Draw the corresponding two-level OR-AND circuit.




OR/AND to NOR/NOR

(Practice Problem #3)

 3. Add bubbles to inputs and bubbles to outputs



 4. Replace all gates with **NOR** gates leaving the gate interconnection unchanged.




Decoders

Design F1 with a Decoder

$$F1 = \sum m(2,3,5,7) - \text{SOM}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or

A	B	C	F1
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

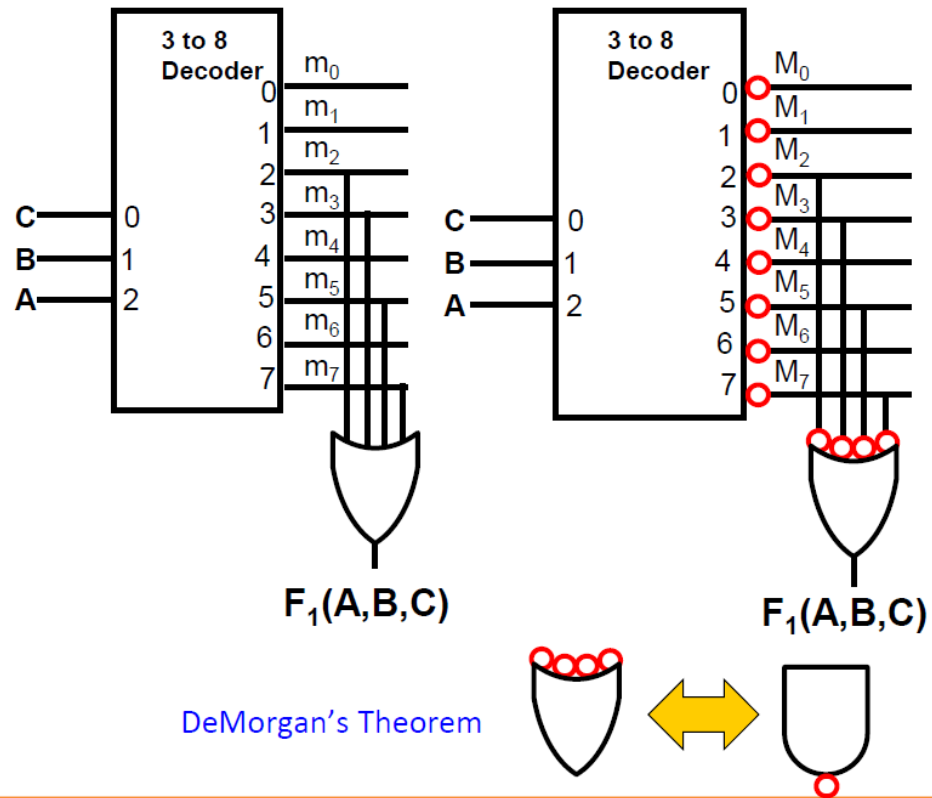

Designing Logic Circuits with MUXs

Technique 1:

- For n variables, use $n-1$ variables as inputs to select lines. Hence, we need a 2^{n-1} -to-1 MUX.

Example: Given $F_1(X,Y,Z) = \Sigma m(1,2,5,7)$, 3 variables so we need a 2^2 -to-1 MUX. Lets allocate X and Y to select lines, leaving Z for the Data Lines.


	X	Y	Z	F	
I_0	0	0	0	0	Z
	0	0	1	1	
I_1	0	1	0	1	Z'
	0	1	1	0	
I_2	1	0	0	0	Z
	1	0	1	1	
I_3	1	1	0	0	Z
	1	1	1	1	

Notice F and Z are the same

Notice F and Z are Complemented




Notice F and Z are the same

Notice F and Z are the same

 

S-R Latch

   Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




\bar{S}	\bar{R}	Q	Q^+
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	—
0	0	1	—

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

NAND function		
X	Y	F_{NAND}
0	0	1
0	1	1
1	0	1
1	1	0

NOTE: any time one of the inputs X or Y is a 0 the output F is a 1.

D-Latch

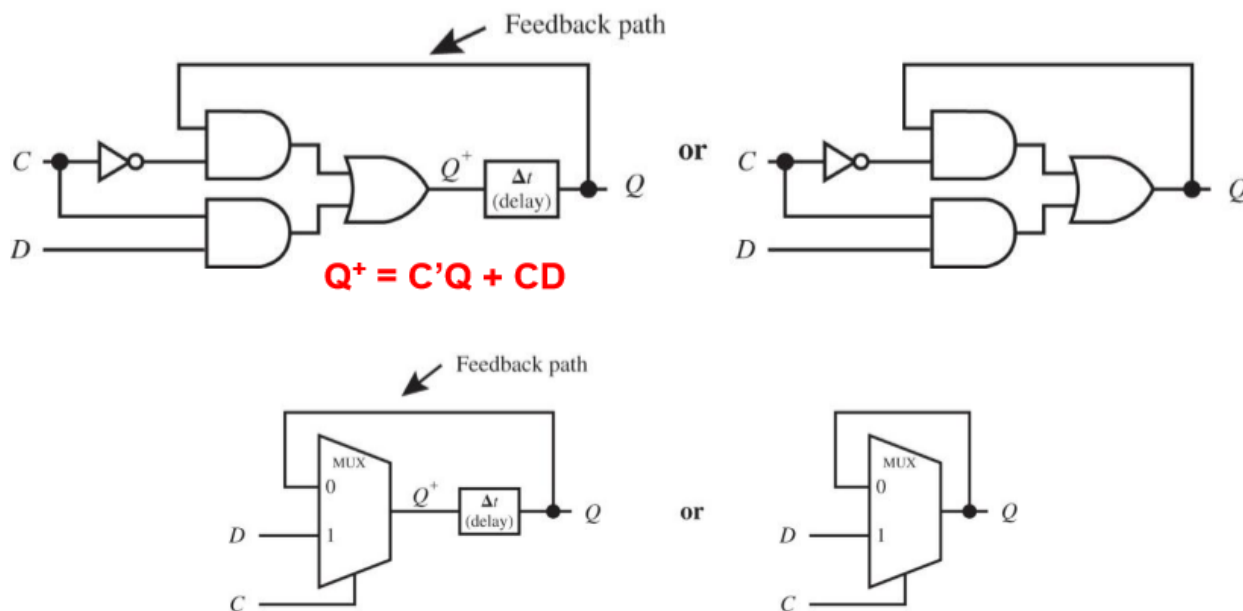

$$Q^+ = C'Q + CD$$

$$\text{2-to-1 MUX Equation: } Z (\text{output}) = A'I_0 + AI_1$$


A is select line, I_0 and I_1 are input lines.

$$Q^+ = C'Q + CD; C = A$$

D-Flip Flop

D Latch with a CLR Input: a) implemented with a logic hazard-free function in AND-OR circuit form, and b) logic symbol

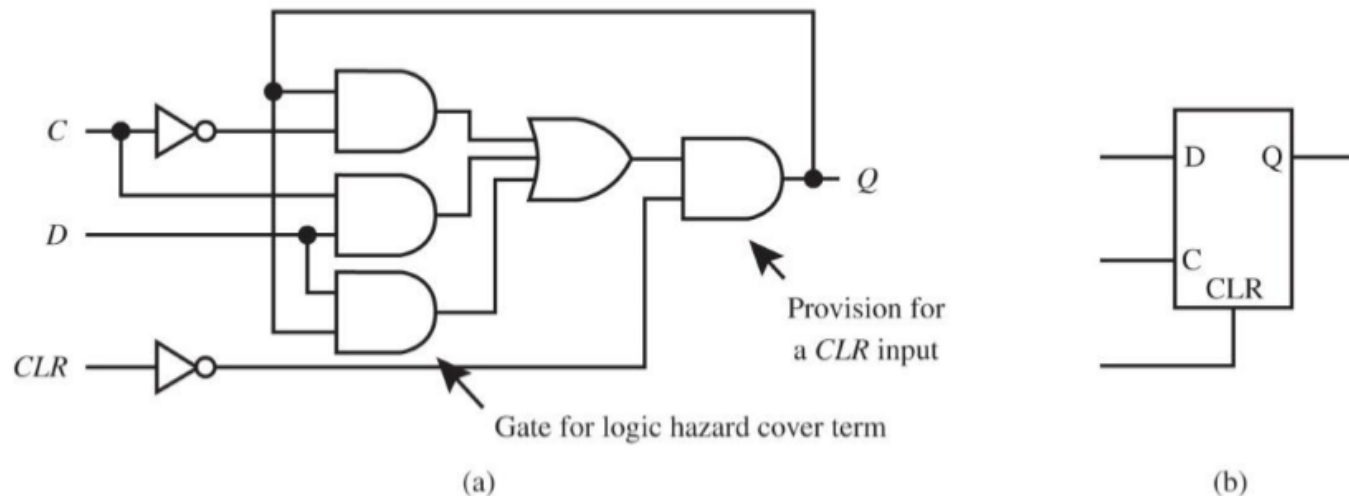Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Extra term removes the logic glitch: $C'Q + CD + DQ$


Counter Design

Binary Up Counter (2 bits):

a) Counting Sequence Diagram

 b) Equivalent State Diagram

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Q&A

