



EGEC 180 – Digital Logic and Computer Structures

Spring 2024

Lecture 14: Analysis and Design of Sequential Circuits (3.4)

Rakesh Mahto, Ph.D.

Office: E 314, California State University, Fullerton

Office Hour: Monday and Wednesday 2:00 - 3:30 pm

Or by appointment

Office Hour Zoom Meeting ID: 891 2907 5346

Email: ramahto@fullerton.edu

Phone No: 657-278-7274

Analysis & Design




Analysis of Clocked Sequential Circuits

The behavior of a sequential circuit is determined by the inputs, outputs and states of its Flip-Flops (FFs).

Analysis: obtain a suitable description (table or diagram) for the time sequence of inputs, outputs and FF states.

- Given a circuit
- Find the State Table or State Diagram

Analysis Model: Two-process PS/NS Method

 


$$Q^+ = T'Q + TQ'$$

$$= Q \oplus T$$

	Q'	Q
T' 0	0	1
T 1	1	0

$$Q^+ = \sum m(1,2)$$

T	Q	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

 


Design of Clocked Sequential Circuits

Design of Sequential Circuit: for its design we need knowledge of the type of FFs used and a list of Boolean functions for the input combinational circuit to the FFs.

- Determine type of FFs (SR, D, T, JK)
- Find combinational circuit connected to input(s) of FFs

Design Model: Two-process PS/NS Method

 


T	Q	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

	Q' = 0	Q = 1
T' = 0	0	1
T = 1	1	0

$$Q^+ = T'Q + TQ'$$

$$= Q \oplus T$$








 


Analysis and Design of Clocked Sequential Circuits

Input equations:

- 1) Part of the circuit that generates the signals for the inputs to the FFs, also
- 2) Selecting the type of FFs.
 - Time is not specified, it is implied
 - Convenient way for specifying the logic diagram also known as state equations

Logic Storage Devices

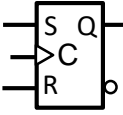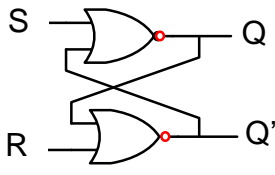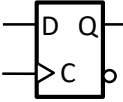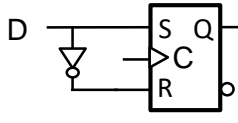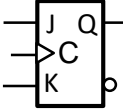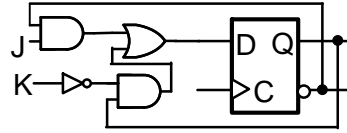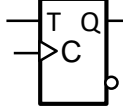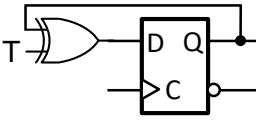Characteristic Table					Excitation Table						
		S	R	Q(t+1)	Operation	Q(t+1) = S + R'Q	Q	Q ⁺	S	R	Operation
		0	0	Q(t)	Hold		0	0	0	d	Hold
		0	1	0	Reset		0	1	1	0	Set
		1	0	1	Set		1	0	0	1	Reset
		1	1	?	Undefined		1	1	d	0	Hold
		D		Q(t+1)	Operation	Q(t+1) = D	Q ⁺		D		Operation
		0		0	Reset		0		0		Reset
		1		1	Set		1		1		Set
		J	K	Q(t+1)	Operation	Q(t+1) = JQ' + K'Q	Q	Q ⁺	J	K	Operation
		0	0	Q(t)	Hold		0	0	0	d	Hold
		0	1	0	Reset		0	1	0	d	Set
		1	0	1	Set		1	0	d	0	Reset
		1	1	Q(t)	Toggle		1	1	d	1	Hold
		T		Q(t+1)	Operation	Q(t+1) = Q ⊕ T	Q ⁺		T		Operation
		0		Q(t)	No Change		Q(t)		0		Hold
		1		Q(t)	Toggle		Q̄(t)		1		Toggle

Analysis and Design of Clocked Sequential Circuits



Inputs, outputs, and FF states may be listed in a State Table or drawn in a State Diagram:

State Table:


Present State (before CLK pulse)			Inputs			Next State (after CLK pulse)			Outputs (during present state)		

Lay this out like you would a truth table

Reading A State Diagram

  

State

 

Transition

1/0

Input (x)   Output(z)


How many Flip-flops do you need?

One per binary digit in a state name
(One per Brain Cell)


Note: **11/00** Implies 2 Inputs and that every state has 4 (2^2) transitions out.
Also, this means there are 2 outputs with each transition.

Moore Models

 Moore Model: Sequential Circuits in which outputs depend on the states, one dimensional column suffices.




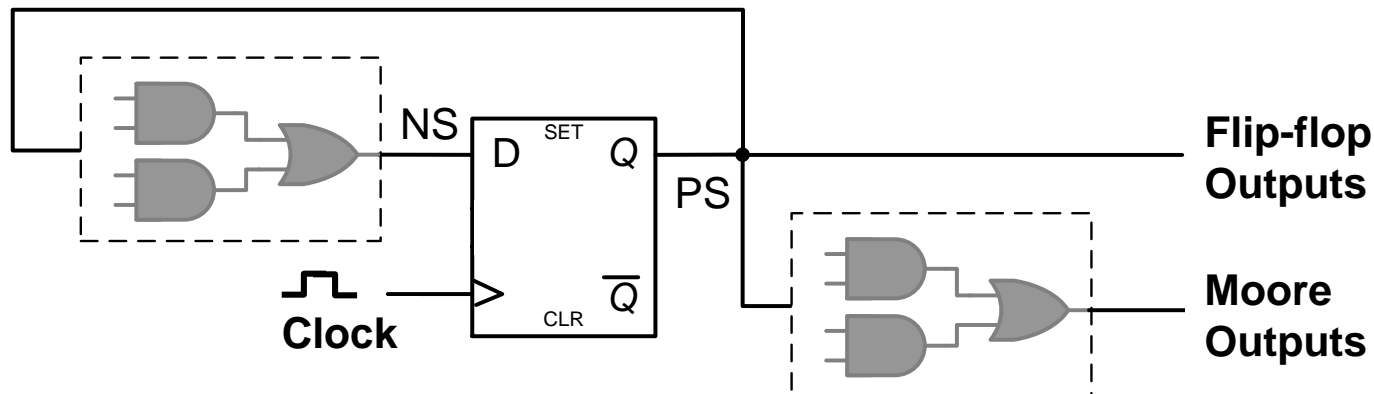NOTE: State Tables and State Diagrams provide the same information.



Mealy Models

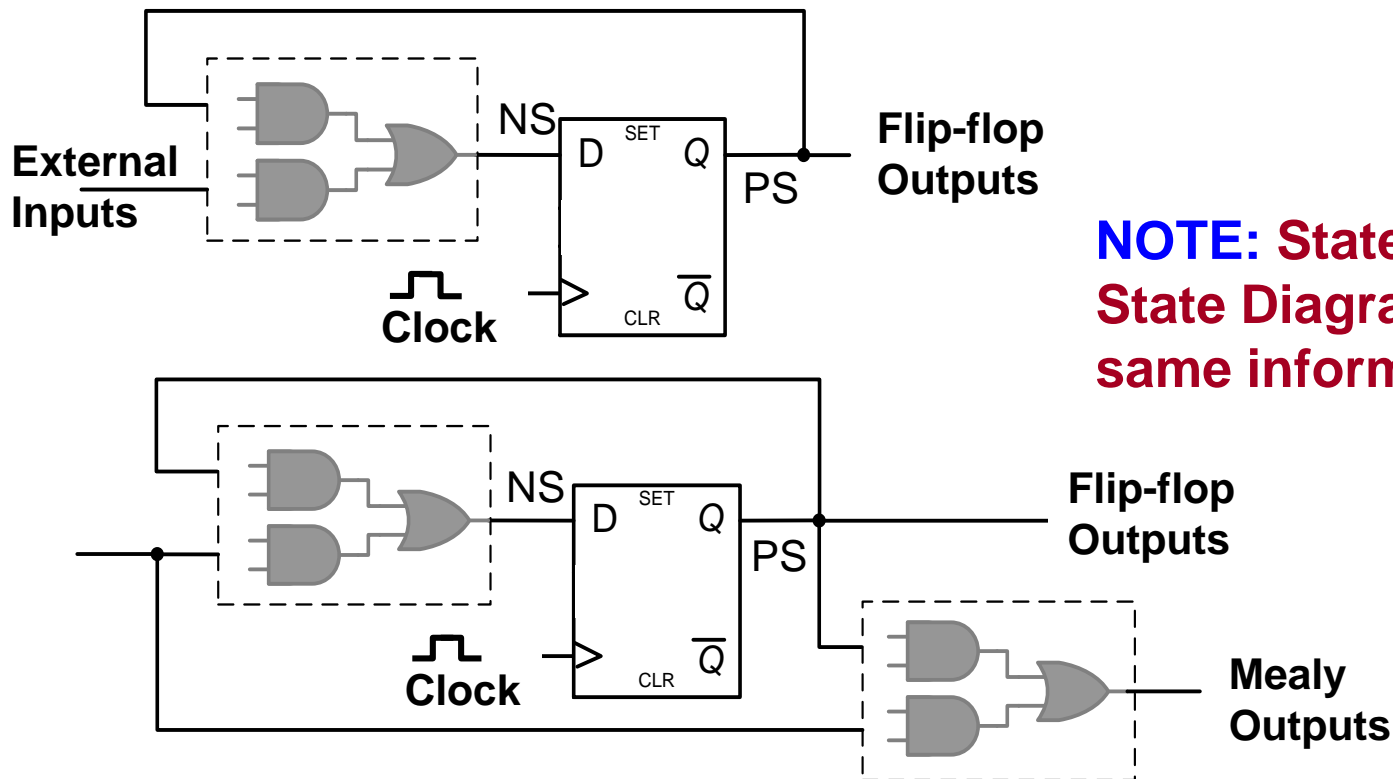Mealy Model: Sequential Circuits in which outputs depend on the inputs and the states, two dimensional columns.




NOTE: State Tables and State Diagrams provide the same information.

Analysis



Analysis of Clocked Sequential Circuits

 Starting with the Logic Diagram (circuit)



NOTE: This is a Mealy Model

Step 1) Write the state, input and output equations

Output equations $F = Q A$

Input equations $E = F + B$

State equations $Q(t+1) = Q^+ = Q A + B$

NOTE:

- 2 inputs – A and B
- 1 Output - F
- 1 D type FF

Analysis of Clocked Sequential Circuits

Step 2) Complete the State Table

Q	Inputs		QA	Q ⁺	F
	A	B			
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	1	1	1
1	1	1	1	1	1


$$Q(t+1) = Q^+ = Q A + B$$

$$F = Q A$$


NOTE: The circled states are considered stable states since the state does not change when transitioning or graphically

AB/F

00/0,
10/0

 

01/0,
10/1,
11/1

 


Analysis of Clocked Sequential Circuits

Step 3) Draw the State Diagram

Q	Inputs		QA	Q ⁺	F
	A	B			
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	1	1	1
1	1	1	1	1	1

AB/F

00/0,
10/0

 

NOTE: There are 2 inputs so each state should have 2^2 outputs and there should be a total of 8 transitions in the diagram one for each row of the state table.

Practice Problem #1

State Table From Equations (1)

$$\begin{aligned} X^+(X,Y,A) &= (((Y+X)'A)') \\ &= (((Y+X)'))' + A' \\ &= Y + X + A' \end{aligned}$$

	Y'A'	Y'A	YA	YA'
	00	01	11	10
X' 0	1	0	1	1
X 1	1	1	1	1

$$X^+ = \sum m(0,2,3,4,5,6,7)$$

$$Y^+(X,Y,A) = A + X'$$

	Y'A'	Y'A	YA	YA'
	00	01	11	10
X' 0	1	1	1	1
X 1	0	1	1	0

$$Y^+ = \sum m(0,1,2,3,5,7)$$

$$\begin{aligned} B^+(X,Y,A) &= A \oplus (Y)' \\ &= AY + A'Y' \end{aligned}$$

	Y'A'	Y'A	YA	YA'
	00	01	11	10
X' 0	1	0	1	0
X 1	1	0	1	0

$$B^+ = \sum m(0,3,4,7)$$

Practice Problem #1

State Table From Equations (2)

Step 2) Complete the State Table

Present State		A	Next State		B
X	Y		X	Y	
0	0	0	1	1	1
0	0	1	0	1	0
0	1	0	1	1	0
0	1	1	1	1	1
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	1	1

$$X^+ = \sum m(0,2,3,4,5,6,7) \quad B^+ = \sum m(1,2,5,6)$$


$$Y^+ = \sum m(0,1,2,3,5,7)$$

NOTE: The circled states are considered stable states since the state does not change when transitioning or graphically

Practice Problem #1

State Table From Equations (3)

Step 3) Draw the State Diagram

 

Present State		A	Next State		B
X	Y		X ⁺	Y ⁺	
0	0	0	1	1	1
0	0	1	0	1	0
0	1	0	1	1	0
0	1	1	1	1	1
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	1	1


Design



Design of Clocked Sequential Circuits

From verbal or written description use this information to generate (in this case the verbal statement said we need to use D flipflops (FF):

 Step 1) Complete State Diagram or State Table



Present State		X	Next State		Z
B	A		B ⁺	A ⁺	
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

Logic Circuit Design

Step 2) Define the FFs inputs so that the State changes occur as specified by problem description. Two approaches:

1. Know FF inputs, want to define the next state. Use Characteristic Table of FFs.
2. Know the transition, want to find the inputs that cause those transitions. Use Excitation Table (PS/NS) of FFs.

Note:

A. Choose types of FFs to use

Number of FFs determined by number of states (4 or 2^2 states = 2 FF)









Type: JK most flexible; SR or D for data transfer; T when complementing is involved. **Most popular** is the D FF.

B. Notation to distinguish FF inputs in complex circuits (2 letter designations)

First letter refers to specific FF input (J, K, D, T, S, R)

Second letter refers to a FF identifier (A, B, C, etc)


Logic Storage Devices

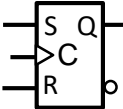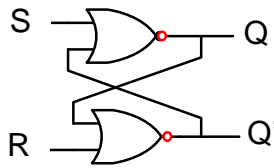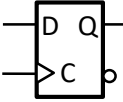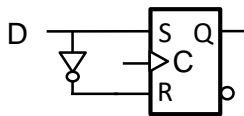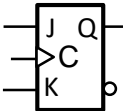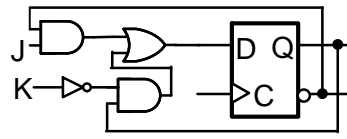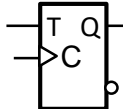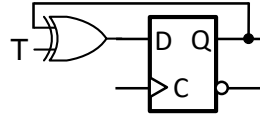Characteristic Table					Excitation Table						
		S	R	Q(t+1)	Operation	Q(t+1) = S + R'Q	Q	Q ⁺	S	R	Operation
		0	0	Q(t)	Hold		0	0	0	d	Hold
		0	1	0	Reset		0	1	1	0	Set
		1	0	1	Set		1	0	0	1	Reset
		1	1	?	Undefined		1	1	d	0	Hold
		D		Q(t+1)	Operation	Q(t+1) = D	Q ⁺		D		Operation
		0		0	Reset		0		0		Reset
		1		1	Set		1		1		Set
		J	K	Q(t+1)	Operation	Q(t+1) = JQ' + K'Q	Q	Q ⁺	J	K	Operation
		0	0	Q(t)	Hold		0	0	0	d	Hold
		0	1	0	Reset		0	1	0	d	Set
		1	0	1	Set		1	0	d	0	Reset
		1	1	Q(t)	Toggle		1	1	d	1	Hold
		T		Q(t+1)	Operation	Q(t+1) = Q ⊕ T	Q ⁺		T		Operation
		0		Q(t)	No Change		Q(t)		0		Hold
		1		Q(t)	Toggle		Q(t)		1		Toggle

Developing Flipflop Input Equations For B⁺ and A⁺


$$B^+ = \bar{B}AX + B(\bar{A}X + AX\bar{X})$$

	AX 00	A'X 01	AX 11	AX' 10
B' 0	0	0	1	0
B 1	0	1	0	1

 

$$A^+ = B\bar{X} + \bar{A}X$$

	AX 00	A'X 01	AX 11	AX' 10
B' 0	0	1	0	0
B 1	1	1	0	1

 


Developing the Output Equation

Present State		X	Next State		Z
B	A		B	A	
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

$$Z = \Sigma m(0,2,3,6,7)$$

	A'X' 00	A'X 01	AX 11	AX' 10
B' 0	1	0	1	1
B 1	0	0	1	1

$$Z = B'X' + A$$

 

Q&A

