



# EGEC 180 – Digital Logic and Computer Structures

Spring 2024

## Final Exam Review

*Rakesh Mahto, Ph.D.*

**Office:** E 314, California State University, Fullerton

**Office Hour:** Monday and Wednesday 2:00 - 3:30 pm

*Or by appointment*

**Office Hour Zoom Meeting ID:** 891 2907 5346

**Email:** [ramahto@fullerton.edu](mailto:ramahto@fullerton.edu)

**Phone No:** 657-278-7274

# Final Exam

- Day: Monday, 13 May 2024
- Time: 11:00 – 12:50 PM
- Lecture Slides from 1 to 14
- Bring a cheat-sheet of one page (A4 Size)- both side, pen, pencil and calculator.

# Conversion

- 8-4-2-1 Code (BCD)
- 6-3-1-1 Code
- Excess-3 Code
- 2-out of 5 Code
- Gray Code
- Binary
- Octal
- Hexadecimal

# Arithmetic Operations

- Adding two Binary, Octal, Hexadecimal number
- Subtraction of two Binary, Octal, Hexadecimal number
- Subtraction using 1's and 2's Complement
- Multiplication
- Division

# Boolean Algebra

- Boolean Functions
- Truth Table
- Logical Circuits
- Minterm
- Maxterm
- K-Map
- Circuit design using NAND Gate and NOR Gate.
- Decoder


# Designing Circuit using NAND or NOR Gate

## OR/AND to NOR/NOR


$$F2 = X'Z' + XZ + Y$$

$$F2' = (X + Y)(X' + Z')Y'$$

 Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



(a)

 

(b)

# Decoders

## Design F1 with a Decoder

$$F1 = \Sigma m(2,3,5,7) - \text{SOM}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

<i>A</i>	<i>B</i>	<i>C</i>	<i>F1</i>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# Designing Logic Circuits with MUXs

## Technique 1:

- For  $n$  variables, use  $n-1$  variables as inputs to select lines. Hence, we need a  $2^{n-1}$ -to-1 MUX.

**Example:** Given  $F_1(X,Y,Z) = \Sigma m(1,2,5,7)$ , 3 variables so we need a  $2^2$ -to-1 MUX. Lets allocate  $X$  and  $Y$  to select lines, leaving  $Z$  for the Data Lines.


	X	Y	Z	F
$I_0$	0	0	0	0
	0	0	1	1
$I_1$	0	1	0	1
	0	1	1	0
$I_2$	1	0	0	0
	1	0	1	1
$I_3$	1	1	0	0
	1	1	1	1

$Z$  Notice  $F$  and  $Z$  are the same

$Z'$  Notice  $F$  and  $Z$  are Complemented

$Z$  Notice  $F$  and  $Z$  are the same




$Z$  Notice  $F$  and  $Z$  are the same

 


   
# S-R Latch

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$\bar{S}$	$\bar{R}$	$Q$	$Q^+$
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	—
0	0	1	—

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

NAND function		
$X$	$Y$	$F_{NAND}$
0	0	1
0	1	1
1	0	1
1	1	0

**NOTE:** any time one of the inputs X or Y is a 0 the output F is a 1.

# D-Latch

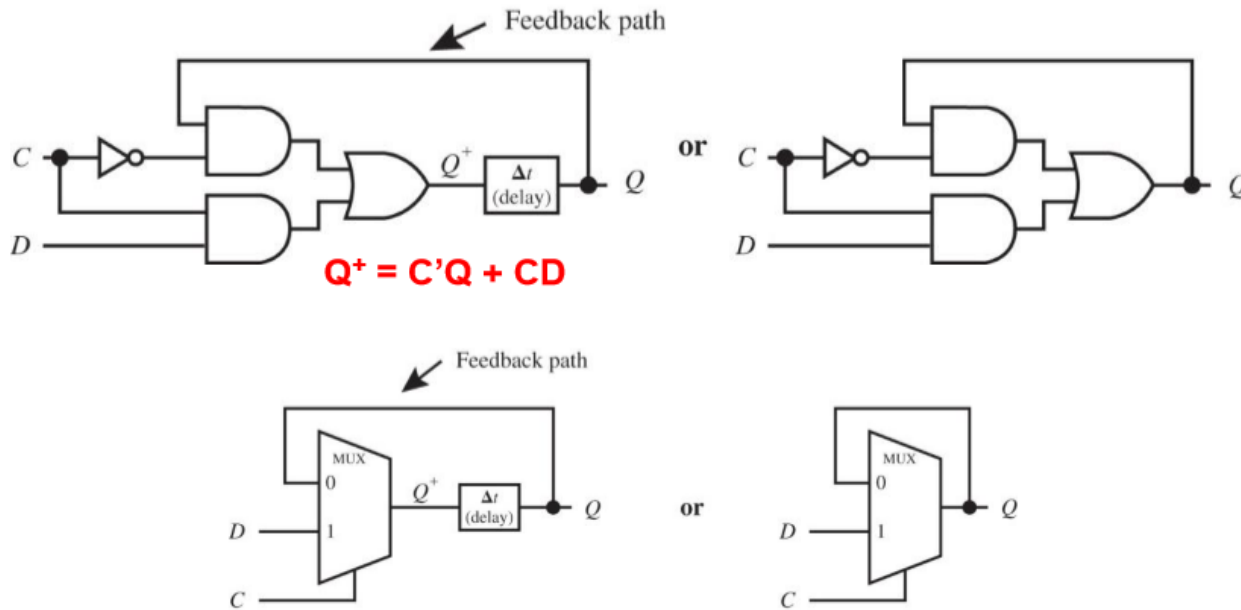

$$Q^+ = C'Q + CD$$

$$\text{2-to-1 MUX Equation: } Z (\text{output}) = A'I_0 + AI_1$$


$A$  is select line,  $I_0$  and  $I_1$  are input lines.

$$Q^+ = C'Q + CD; C = A$$

# D-Flip Flop

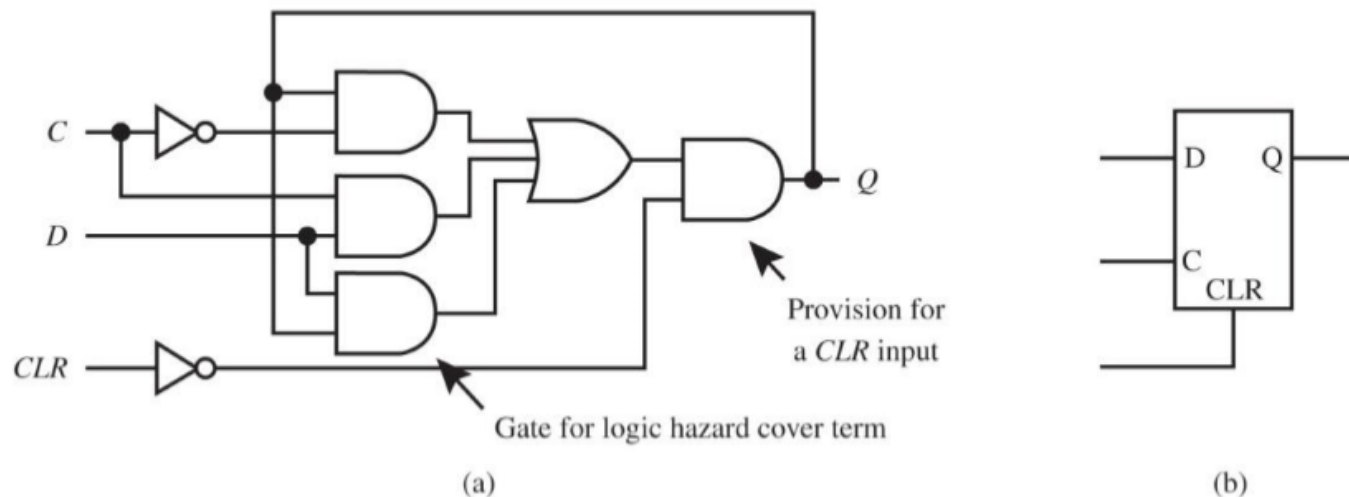**D Latch with a CLR Input: a) implemented with a logic hazard-free function in AND-OR circuit form, and b) logic symbol**


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Extra term removes the logic glitch:  $C'Q + CD + DQ$

# Mealy State Machine Analysis
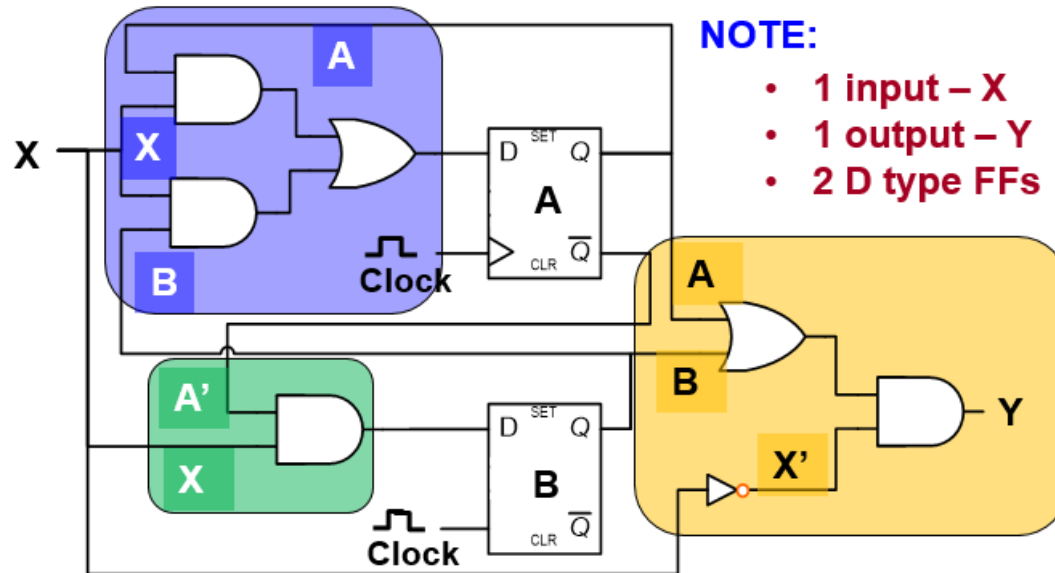
## Starting with the Logic Diagram (circuit)



**NOTE:**

- 1 input – X
- 1 output – Y
- 2 D type FFs

**NOTE:** This is a Mealy Model

**Step 1) Write the state, input and output equations**

**Output equations**

**Input equations**


$$Y = (A + B)X'$$

$$A^+ = AX + BX$$

$$B^+ = A'X$$

# Mealy State Machine Analysis (Continue)


## Step 3) Draw the State Diagram

 


Present State		X	Next State		Y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

# Mealy State Machine Design

## State Diagram to Design

 

# Mealy State Machine Design (Continue)

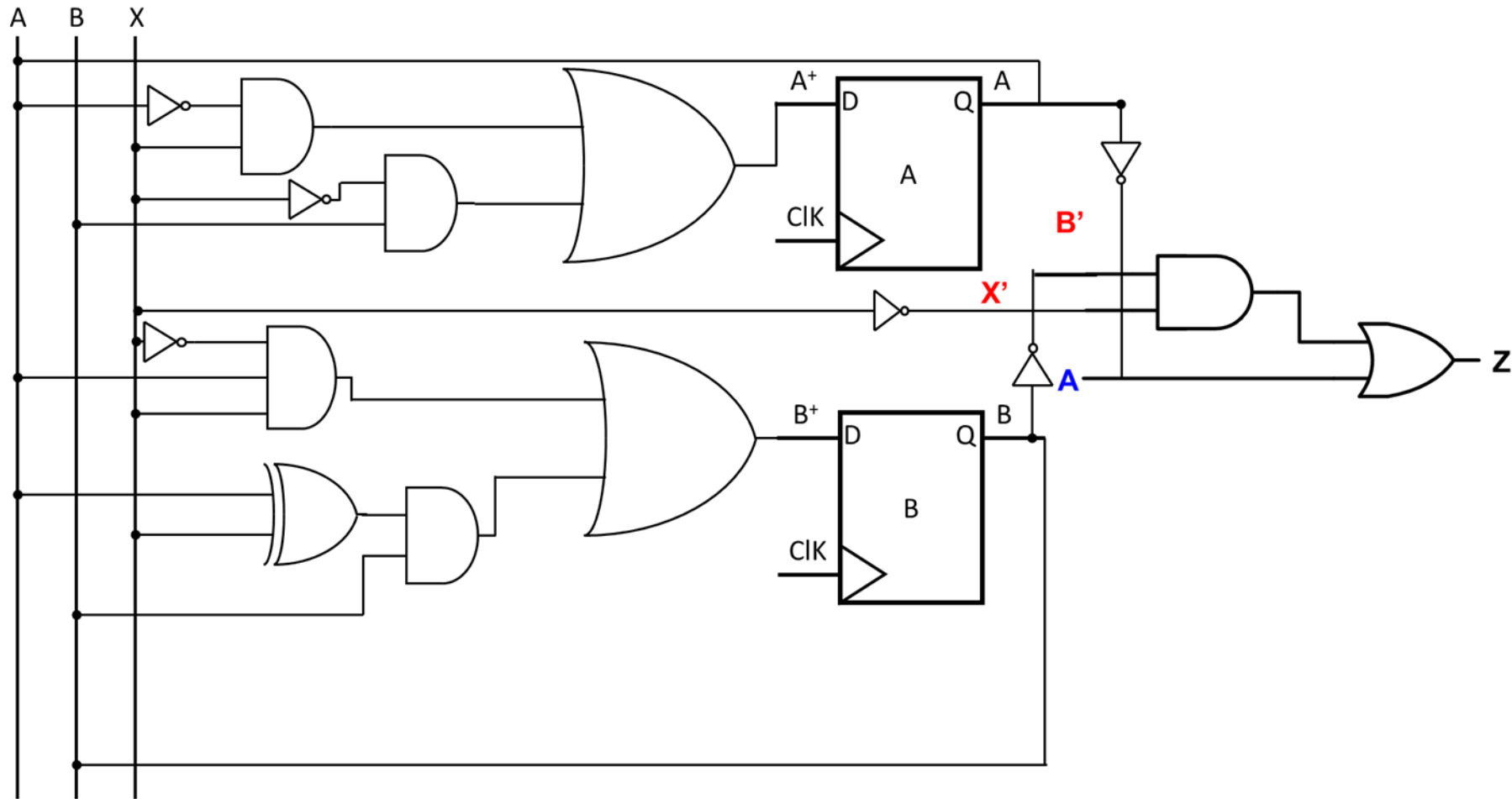

# Q&A

