



# EGEC 180 – Digital Logic and Computer Structures

Spring 2024

## Lecture 8: Designing Circuits in AND/NAND and OR/NOR(2.3.3)

*Rakesh Mahto, Ph.D.*

**Office:** E 314, California State University, Fullerton

**Office Hour:** Monday and Wednesday 2:00 - 3:30 pm

*Or by appointment*

**Office Hour Zoom Meeting ID:** 891 2907 5346

**Email:** [ramahto@fullerton.edu](mailto:ramahto@fullerton.edu)

**Phone No:** 657-278-7274

# Designing Circuits in NAND/NAND and NOR/NOR Form





# DeMorgan's Theorem





$$X.Y = (X' + Y')'$$

$$(X.Y)' = X' + Y'$$

  

$$X + Y = (X'.Y')'$$


$$(X+Y)' = X'.Y'$$

  

# Equivalent Gate Circuits

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Equivalent gate circuits


 


# DeMorgan Rules

## Graphical Symbols


To obtain a De Morgan equivalent gate symbol for an AND, OR, NAND, or NOR gate:

  1. Add bubbles to all inputs and bubbles to all outputs




Double Negation

 2. Change **ANDs** to **ORs** and Change **ORs** to **ANDs**



Double Negation

 3. Two bubbles result in no bubble; Double Negation Theorem




# Example Problem #1

## Graphical DeMorgan's


To obtain a De Morgan equivalent gate symbol for an AND, OR, NAND, or NOR gate:

 1. Add bubbles to all inputs and bubbles to all outputs



2. Change **ANDs** to **ORs** and Change **ORs** to **ANDs**

 3. Two bubbles result in no bubble; Double Negation Theorem




# DeMorgan's Theorem

## Practice Problem #1

Given the following truth function  $F_1(A,B,C,D) = ABC' + ABCD' + BCD$

$$F_1(A,B,C,D) = AB + BCD$$



		CD			
		C'D' 00	C'D 01	CD 11	CD' 10
AB	A'B' 00	0	0	0	0
	A'B 01	0	0	1	0
	AB 11	1	1	1	1
	AB' 10	0	0	0	0

 

# Practice Problem #1


## Graphical DeMorgan's

  1. Add bubbles to all inputs and bubbles to all outputs



2. Change **ANDs** to **ORs** and Change **ORs** to **ANDs**

3. Apply Double Negation Theorem

 


$$F_1(A,B,C,D) = [(A' + B')(B' + C' + D')]'$$




 
# Two-Level Gate Circuits

The maximum number of gates cascaded in series between a circuit input and output is referred to as the number of levels.



  A function written in **SOPs** form or **POSs** form corresponds directly to a **two-level gate circuit**.





We assume that all literals are available as circuit inputs. Inverters used to form the variable complements are not counted when determining the number of levels in a circuit.

# AND-OR to NAND-NAND Transformation


*Procedure for designing a minimum two-level NAND-NAND circuit:*

  1. Find a minimum *sum-of-products* expression for **F** using a Karnaugh Map
2. Draw the corresponding two-level **AND-OR** circuit.
3. Add bubbles to inputs and bubbles to outputs



# AND-OR to NAND-NAND Transformation

 4. Replace all gates with **NAND** gates leaving the gate interconnection unchanged.



# AND-OR to NAND-NAND Transformation

## (Practice Problem #2)


Given  $F_2(A,B,C,D) = A'B'C' + BD' + AC'$

- Find a minimum *sum-of-products* expression for F using a Karnaugh Map

		CD			
		C'D'	C'D	CD	CD'
AB	A'B'	00	01	11	10
	A'B	00	01	11	10
	AB	00	01	11	10
	AB'	00	01	11	10


$$F_2(A,B,C,D) = B'C' + BD' + AC'$$

 - Draw the corresponding two-level AND-OR circuit.




# AND-OR to NAND-NAND Transformation

 3. Add bubbles to inputs and bubbles to outputs




 
4. Replace all gates with **NAND** gates leaving the gate interconnection unchanged.



# OR-AND to NOR-NOR Transformation


*Procedure for designing a minimum two-level NAND-NAND circuit:*

  1. Find a minimum *product-of-sum* expression for **F** using a Karnaugh Map
2. Draw the corresponding two-level **OR - AND** circuit.
3. Add bubbles to inputs and bubbles to outputs



# OR-AND to NOR-NOR Transformation

 4. Replace all gates with **NOR** gates leaving the gate interconnection unchanged.



# OR/AND to NOR/NOR

## (Practice Problem #3)


Given  $F_2(X,Y,Z) = X'Z' + XZ + Y$

1. Find a minimum *product-of-sum* expression for F using a Karnaugh Map

		YZ			
		Y'Z'	Y'Z	YZ	YZ'
X	X'	00	01	11	10
	0	1	0	1	1
X	1	0	1	1	1

$$F_2(X,Y,Z) = (X+Y+Z')(X'+Y+Z)$$

 2. Draw the corresponding two-level OR-AND circuit.







# OR/AND to NOR/NOR

## (Practice Problem #3)

 3. Add bubbles to inputs and bubbles to outputs



 4. Replace all gates with **NOR** gates leaving the gate interconnection unchanged.



# Q&A

